

Chapter 2

1. The load line will intersect at $I_D = \frac{E}{R} = \frac{12 \text{ V}}{750 \Omega} = 16 \text{ mA}$ and $V_D = 12 \text{ V}$.

(a) $V_{D_Q} \cong \mathbf{0.85 \text{ V}}$

$I_{D_Q} \cong \mathbf{15 \text{ mA}}$

$$V_R = E - V_{D_Q} = 12 \text{ V} - 0.85 \text{ V} = \mathbf{11.15 \text{ V}}$$

(b) $V_{D_Q} \cong \mathbf{0.7 \text{ V}}$

$I_{D_Q} \cong \mathbf{15 \text{ mA}}$

$$V_R = E - V_{D_Q} = 12 \text{ V} - 0.7 \text{ V} = \mathbf{11.3 \text{ V}}$$

(c) $V_{D_Q} \cong \mathbf{0 \text{ V}}$

$I_{D_Q} \cong \mathbf{16 \text{ mA}}$

$$V_R = E - V_{D_Q} = 12 \text{ V} - 0 \text{ V} = \mathbf{12 \text{ V}}$$

For (a) and (b), levels of V_{D_Q} and I_{D_Q} are quite close. Levels of part (c) are reasonably close but as expected due to level of applied voltage E .

2. (a) $I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.2 \text{ k}\Omega} = 30 \text{ mA}$

The load line extends from $I_D = 30 \text{ mA}$ to $V_D = 6 \text{ V}$.

$V_{D_Q} \cong \mathbf{0.95 \text{ V}}, I_{D_Q} \cong \mathbf{25.3 \text{ mA}}$

(b) $I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.47 \text{ k}\Omega} = 12.77 \text{ mA}$

The load line extends from $I_D = 12.77 \text{ mA}$ to $V_D = 6 \text{ V}$.

$V_{D_Q} \cong \mathbf{0.8 \text{ V}}, I_{D_Q} \cong \mathbf{11 \text{ mA}}$

(c) $I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.68 \text{ k}\Omega} = 8.82 \text{ mA}$

The load line extends from $I_D = 8.82 \text{ mA}$ to $V_D = 6 \text{ V}$.

$V_{D_Q} \cong \mathbf{0.78 \text{ V}}, I_{D_Q} \cong \mathbf{78 \text{ mA}}$

The resulting values of V_{D_Q} are quite close, while I_{D_Q} extends from 7.8 mA to 25.3 mA.

3. Load line through $I_{D_Q} = 10 \text{ mA}$ of characteristics and $V_D = 7 \text{ V}$ will intersect I_D axis as 11.3 mA.

$$I_D = 11.3 \text{ mA} = \frac{E}{R} = \frac{7 \text{ V}}{R}$$

$$\text{with } R = \frac{7 \text{ V}}{11.3 \text{ mA}} = 619.47 \text{ k}\Omega \cong \mathbf{0.62 \text{ k}\Omega \text{ standard resistor}}$$

4. (a) $I_D = I_R = \frac{E - V_D}{R} = \frac{30 \text{ V} - 0.7 \text{ V}}{1.5 \text{ k}\Omega} = 19.53 \text{ mA}$
 $V_D = 0.7 \text{ V}, V_R = E - V_D = 30 \text{ V} - 0.7 \text{ V} = 29.3 \text{ V}$

(b) $I_D = \frac{E - V_D}{R} = \frac{30 \text{ V} - 0 \text{ V}}{1.5 \text{ k}\Omega} = 20 \text{ mA}$
 $V_D = 0 \text{ V}, V_R = 30 \text{ V}$

Yes, since $E \gg V_T$ the levels of I_D and V_R are quite close.

5. (a) $I = 0 \text{ mA};$ diode reverse-biased.

(b) $V_{20\Omega} = 20 \text{ V} - 0.7 \text{ V} = 19.3 \text{ V}$ (Kirchhoff's voltage law)

$$I(20 \Omega) = \frac{19.3 \text{ V}}{20 \Omega} = 0.965 \text{ A}$$

$$V(10 \Omega) = 20 \text{ V} - 0.7 \text{ V} = 19.3 \text{ V}$$

$$I(10 \Omega) = \frac{19.3 \text{ V}}{10 \Omega} = 1.93 \text{ A}$$

$$I = I(10 \Omega) + I(20 \Omega) \\ = 2.895 \text{ A}$$

(c) $I = \frac{10 \text{ V}}{10 \Omega} = 1 \text{ A};$ center branch open

6. (a) Diode forward-biased,

Kirchhoff's voltage law (CW): $-5 \text{ V} + 0.7 \text{ V} - V_o = 0$
 $V_o = -4.3 \text{ V}$

$$I_R = I_D = \frac{|V_o|}{R} = \frac{4.3 \text{ V}}{2.2 \text{ k}\Omega} = 1.955 \text{ mA}$$

(b) Diode forward-biased,

$$I_D = \frac{8 \text{ V} + 6 \text{ V} - 0.7 \text{ V}}{1.2 \text{ k}\Omega + 4.7 \text{ k}\Omega} = 2.25 \text{ mA}$$


$$V_o = 8 \text{ V} - (2.25 \text{ mA})(1.2 \text{ k}\Omega) = 5.3 \text{ V}$$

7. (a) $V_o = \frac{10 \text{ k}\Omega(12 \text{ V} - 0.7 \text{ V} - 0.3 \text{ V})}{2 \text{ k}\Omega + 10 \text{ k}\Omega} = 9.17 \text{ V}$
(b) $V_o = 10 \text{ V}$

8. (a) Determine the Thevenin equivalent circuit for the 10 mA source and 2.2 kΩ resistor.

$$E_{Th} = IR = (10 \text{ mA})(2.2 \text{ k}\Omega) = 22 \text{ V}$$

$$R_{Th} = 2.2 \text{ k}\Omega$$

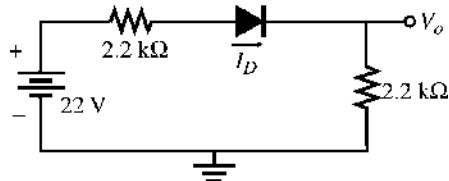

Diode forward-biased

$$I_D = \frac{22 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 4.84 \text{ mA}$$

$$\begin{aligned} V_o &= I_D(1.2 \text{ k}\Omega) \\ &= (4.84 \text{ mA})(1.2 \text{ k}\Omega) \\ &= 5.81 \text{ V} \end{aligned}$$

- (b) Diode forward-biased

$$I_D = \frac{20 \text{ V} + 20 \text{ V} - 0.7 \text{ V}}{6.8 \text{ k}\Omega} = 5.78 \text{ mA}$$

Kirchhoff's voltage law (CW):

$$+V_o - 0.7 \text{ V} + 20 \text{ V} = 0$$

$$V_o = -19.3 \text{ V}$$

9. (a) $V_{o_1} = 12 \text{ V} - 0.7 \text{ V} = 11.3 \text{ V}$

$$V_{o_2} = 1.2 \text{ V}$$

- (b) $V_{o_1} = 0 \text{ V}$

$$V_{o_2} = 0 \text{ V}$$

10. (a) Both diodes forward-biased

Si diode turns on first and locks in 0.7 V drop.

$$I_R = \frac{12 \text{ V} - 0.7 \text{ V}}{4.7 \text{ k}\Omega} = 2.4 \text{ mA}$$

$$I_D = I_R = 2.4 \text{ mA}$$

$$V_o = 12 \text{ V} - 0.7 \text{ V} = 11.3 \text{ V}$$

- (b) Right diode forward-biased:

$$I_D = \frac{20 \text{ V} + 4 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega} = 10.59 \text{ mA}$$

$$V_o = 20 \text{ V} - 0.7 \text{ V} = 19.3 \text{ V}$$

11. (a) Si diode “on” preventing GaAs diode from turning “on”:

$$I = \frac{1 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = \frac{0.3 \text{ V}}{1 \text{ k}\Omega} = 0.3 \text{ mA}$$

$$V_o = 1 \text{ V} - 0.7 \text{ V} = 0.3 \text{ V}$$

$$(b) I = \frac{16 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V} + 4 \text{ V}}{4.7 \text{ k}\Omega} = \frac{18.6 \text{ V}}{4.7 \text{ k}\Omega} = 3.96 \text{ mA}$$

$$V_o = 16 \text{ V} - 0.7 \text{ V} - 0.7 \text{ V} = 14.6 \text{ V}$$

12. Both diodes forward-biased:


$$V_{o_1} = 0.7 \text{ V}, V_{o_2} = 0.7 \text{ V}$$

$$I_{1 \text{ k}\Omega} = \frac{20 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega} = \frac{19.3 \text{ V}}{1 \text{ k}\Omega} = 19.3 \text{ mA}$$

$$I_{0.47 \text{ k}\Omega} = 0 \text{ mA}$$

$$I = I_{1 \text{ k}\Omega} - I_{0.47 \text{ k}\Omega} = 19.3 \text{ mA} - 0 \text{ mA} \\ = \mathbf{19.3 \text{ mA}}$$

13.

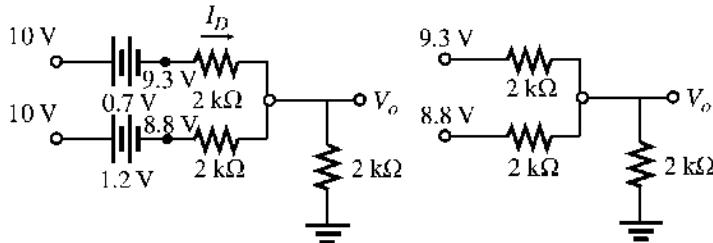

$$\text{Superposition: } V_{o_1} (9.3 \text{ V}) = \frac{1 \text{ k}\Omega (9.3 \text{ V})}{1 \text{ k}\Omega + 2 \text{ k}\Omega} = 3.1 \text{ V}$$

$$V_{o_2} (8.8 \text{ V}) = \frac{16 \text{ k}\Omega (8.8 \text{ V})}{1 \text{ k}\Omega + 2 \text{ k}\Omega} = 2.93 \text{ V}$$

$$V_o = V_{o_1} + V_{o_2} = \mathbf{6.03 \text{ V}}$$

$$I_D = \frac{9.3 \text{ V} - 6.03 \text{ V}}{2 \text{ k}\Omega} = \mathbf{1.635 \text{ mA}}$$

14. Both diodes “off”. The threshold voltage of 0.7 V is unavailable for either diode.

$$V_o = \mathbf{0 \text{ V}}$$

15. Both diodes “on”, $V_o = 10 \text{ V} - 0.7 \text{ V} = \mathbf{9.3 \text{ V}}$

16. Both diodes “on”.

$$V_o = \mathbf{0.7 \text{ V}}$$

17. Both diodes “off”, $V_o = \mathbf{10 \text{ V}}$

18. The Si diode with -5 V at the cathode is “on” while the other is “off”. The result is

$$V_o = -5 \text{ V} + 0.7 \text{ V} = \mathbf{-4.3 \text{ V}}$$

19. 0 V at one terminal is “more positive” than -5 V at the other input terminal. Therefore assume lower diode “on” and upper diode “off”.

The result:

$$V_o = 0 \text{ V} - 0.7 \text{ V} = \mathbf{-0.7 \text{ V}}$$

The result supports the above assumptions.

20. Since all the system terminals are at 10 V the required difference of 0.7 V across either diode cannot be established. Therefore, both diodes are “off” and

$$V_o = \mathbf{+10 \text{ V}}$$

as established by 10 V supply connected to 1 kΩ resistor.

21. The Si diode requires more terminal voltage than the Ge diode to turn “on”. Therefore, with 5 V at both input terminals, assume Si diode “off” and Ge diode “on”.


The result: $V_o = 5 \text{ V} - 0.3 \text{ V} = \mathbf{4.7 \text{ V}}$

The result supports the above assumptions.

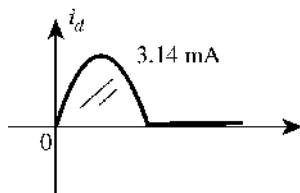
22. $V_{dc} = 0.318 \text{ V}_m \Rightarrow V_m = \frac{V_{dc}}{0.318} = \frac{2 \text{ V}}{0.318} = \mathbf{6.28 \text{ V}}$



$$I_m = \frac{V_m}{R} = \frac{6.28 \text{ V}}{2 \text{ k}\Omega} = \mathbf{3.14 \text{ mA}}$$



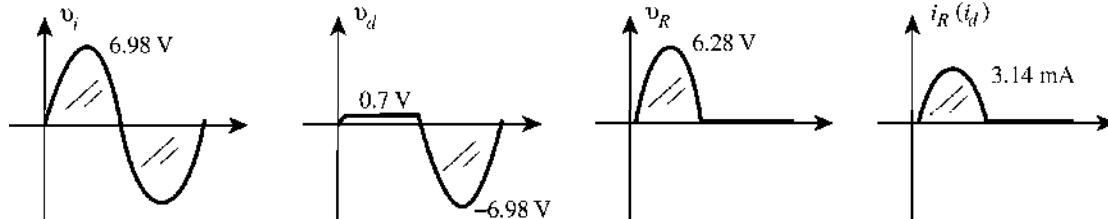
23. Using $V_{dc} \approx 0.318(V_m - V_T)$
 $2 \text{ V} = 0.318(V_m - 0.7 \text{ V})$
Solving: $V_m = \mathbf{6.98 \text{ V}} \approx 10:1$ for $V_m:V_T$



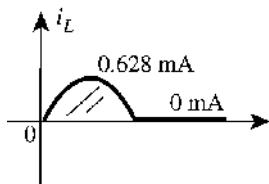24. $V_m = \frac{V_{dc}}{0.318} = \frac{2 \text{ V}}{0.318} = \mathbf{6.28 \text{ V}}$




$$I_{L_{\max}} = \frac{6.28 \text{ V}}{10 \text{ k}\Omega} = \mathbf{0.628 \text{ mA}}$$




$$I_{\max}(2 \text{ k}\Omega) = \frac{6.28 \text{ V}}{2 \text{ k}\Omega} = 3.14 \text{ mA}$$
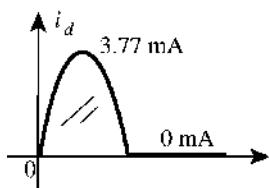
$$I_{D_{\max}} = I_{L_{\max}} + I_{\max}(2 \text{ k}\Omega) = 0.678 \text{ mA} + 3.14 \text{ mA} = 3.77 \text{ mA}$$



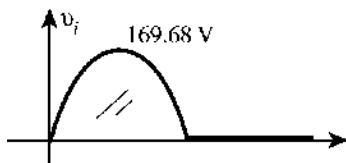25. $V_m = \sqrt{2} (120 \text{ V}) = 169.68 \text{ V}$
 $V_{dc} = 0.318V_m = 0.318(169.68 \text{ V}) = 53.96 \text{ V}$



26. Diode will conduct when $v_o = 0.7 \text{ V}$; that is,

$$v_o = 0.7 \text{ V} = \frac{1 \text{ k}\Omega(v_i)}{1 \text{ k}\Omega + 1 \text{ k}\Omega}$$

Solving: $v_i = 1.4 \text{ V}$

For $v_i \geq 1.4 \text{ V}$ Si diode is “on” and $v_o = 0.7 \text{ V}$.

For $v_i < 1.4 \text{ V}$ Si diode is open and level of v_o is determined by voltage divider rule:

$$v_o = \frac{1 \text{ k}\Omega(v_i)}{1 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.5 v_i$$



For $v_i = -10 \text{ V}$:

$$v_o = 0.5(-10 \text{ V}) \\ = -5 \text{ V}$$

When $v_o = 0.7 \text{ V}$, $v_{R_{\max}} = v_{i_{\max}} - 0.7 \text{ V}$

$$= 10 \text{ V} - 0.7 \text{ V} = 9.3 \text{ V}$$
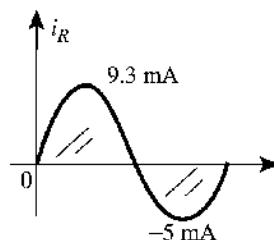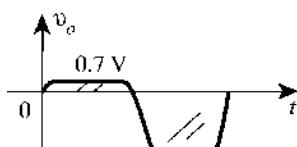
$$I_{R_{\max}} = \frac{9.3 \text{ V}}{1 \text{ k}\Omega} = 9.3 \text{ mA}$$



$$I_{\max(\text{reverse})} = \frac{10 \text{ V}}{1 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.5 \text{ mA}$$

27. (a) $P_{\max} = 14 \text{ mW} = (0.7 \text{ V})I_D$

$$I_D = \frac{14 \text{ mW}}{0.7 \text{ V}} = 20 \text{ mA}$$

(b) $I_{\max} = 2 \times 20 \text{ mA} = 40 \text{ mA}$

(c) $4.7 \text{ k}\Omega \parallel 68 \text{ k}\Omega = 4.4 \text{ k}\Omega$

$$V_R = 160 \text{ V} - 0.7 \text{ V} = 159.3 \text{ V}$$

$$I_{\max} = \frac{159.3 \text{ V}}{4.4 \text{ k}\Omega} = 36.2 \text{ mA}$$

$$I_d = \frac{I_{\max}}{2} = 18.1 \text{ mA}$$

(d) Total damage, **36.2 mA > 20 mA**

28. (a) $V_m = \sqrt{2} (120 \text{ V}) = 169.7 \text{ V}$


$$\begin{aligned} V_{L_m} &= V_{i_m} - 2V_D \\ &= 169.7 \text{ V} - 2(0.7 \text{ V}) = 169.7 \text{ V} - 1.4 \text{ V} \\ &= 168.3 \text{ V} \\ V_{dc} &= 0.636(168.3 \text{ V}) = 107.04 \text{ V} \end{aligned}$$

(b) PIV = $V_m(\text{load}) + V_D = 168.3 \text{ V} + 0.7 \text{ V} = 169 \text{ V}$

(c) $I_D(\max) = \frac{V_{L_m}}{R_L} = \frac{168.3 \text{ V}}{1 \text{ k}\Omega} = 168.3 \text{ mA}$


(d) $P_{\max} = V_D I_D = (0.7 \text{ V})I_{\max}$
 $= (0.7 \text{ V})(168.3 \text{ mA})$
= 117.81 mW

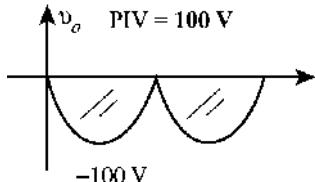29. $v_o \quad \text{PIV} = 100 \text{ V}$





$$I_{\max} = \frac{100 \text{ V}}{2.2 \text{ k}\Omega} = 45.45 \text{ mA}$$

30. Positive half-cycle of v_i :

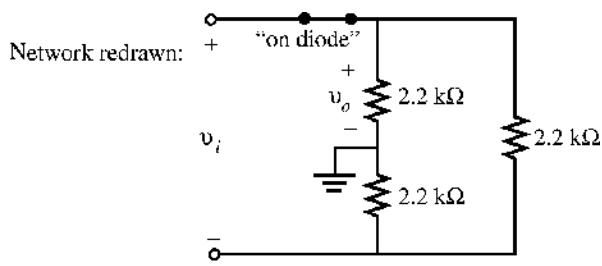

Negative half-cycle of v_i :

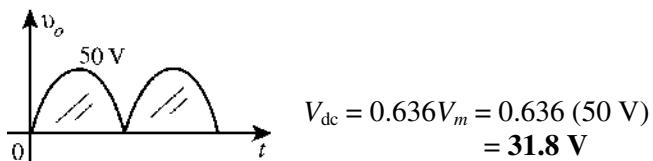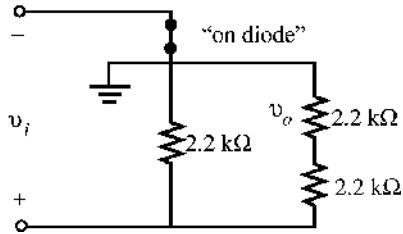

$$V_{dc} = 0.636V_m = 0.636(50 \text{ V}) = 31.8 \text{ V}$$

31. Positive pulse of v_i :

Top left diode “off”, bottom left diode “on”

$$2.2 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.1 \text{ k}\Omega$$

$$V_{o_{peak}} = \frac{1.1 \text{ k}\Omega(170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$

Negative pulse of v_i :

Top left diode “on”, bottom left diode “off”

$$V_{o_{peak}} = \frac{1.1 \text{ k}\Omega(170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$


$$V_{dc} = 0.636(56.67 \text{ V}) = 36.04 \text{ V}$$

32. (a) Si diode open for positive pulse of v_i and $v_o = 0 \text{ V}$

For $-20 \text{ V} < v_i \leq -0.7 \text{ V}$ diode “on” and $v_o = v_i + 0.7 \text{ V}$.

$$\text{For } v_i = -20 \text{ V}, v_o = -20 \text{ V} + 0.7 \text{ V} = -19.3 \text{ V}$$
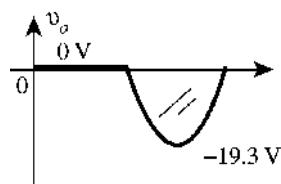
$$\text{For } v_i = -0.7 \text{ V}, v_o = -0.7 \text{ V} + 0.7 \text{ V} = 0 \text{ V}$$



Voltage-divider rule:

$$\begin{aligned} V_{o_{max}} &= \frac{2.2 \text{ k}\Omega(V_{i_{max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2}(V_{i_{max}}) \\ &= \frac{1}{2}(100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$

Polarity of v_o across the $2.2 \text{ k}\Omega$ resistor acting as a load is the same.

Voltage-divider rule:

$$\begin{aligned} V_{o_{max}} &= \frac{2.2 \text{ k}\Omega(V_{i_{max}})}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} \\ &= \frac{1}{2}(V_{i_{max}}) \\ &= \frac{1}{2}(100 \text{ V}) \\ &= 50 \text{ V} \end{aligned}$$

- (b) For $v_i \leq 8$ V the 8 V battery will ensure the diode is forward-biased and $v_o = v_i - 8$ V.


At $v_i = 8$ V

$$v_o = 8 \text{ V} - 8 \text{ V} = \mathbf{0 \text{ V}}$$

At $v_i = -20$ V

$$v_o = -20 \text{ V} - 8 \text{ V} = \mathbf{-28 \text{ V}}$$

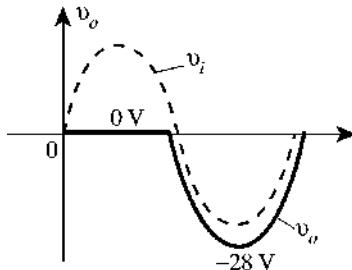For $v_i > 8$ V the diode is reverse-biased and $v_o = \mathbf{0 \text{ V}}$.



33. (a) Positive pulse of v_i :

$$V_o = \frac{1.8 \text{ k}\Omega(12 \text{ V} - 0.7 \text{ V})}{1.8 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \mathbf{5.09 \text{ V}}$$

Negative pulse of v_i :


diode “open”, $v_o = \mathbf{0 \text{ V}}$

- (b) Positive pulse of v_i :

$$V_o = 12 \text{ V} - 0.7 \text{ V} + 4 \text{ V} = \mathbf{15.3 \text{ V}}$$

Negative pulse of v_i :

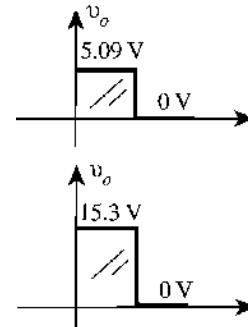diode “open”, $v_o = \mathbf{0 \text{ V}}$




34. (a) For $v_i = 20$ V the diode is reverse-biased and $v_o = \mathbf{0 \text{ V}}$.

For $v_i = -5$ V, v_i overpowers the 4 V battery and the diode is “on”.


Applying Kirchhoff's voltage law in the clockwise direction:
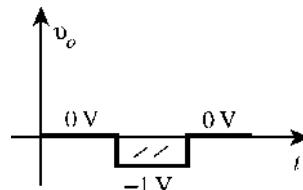
$$-5 \text{ V} + 4 \text{ V} - v_o = 0 \\ v_o = \mathbf{-1 \text{ V}}$$



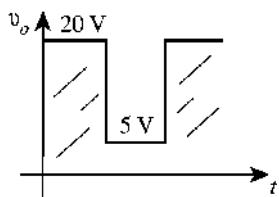- (b) For $v_i = 20$ V the 20 V level overpowers the 5 V supply and the diode is “on”. Using the short-circuit equivalent for the diode we find $v_o = v_i = \mathbf{20 \text{ V}}$.


For $v_i = -5$ V, both v_i and the 5 V supply reverse-bias the diode and separate v_i from v_o . However, v_o is connected directly through the $2.2 \text{ k}\Omega$ resistor to the 5 V supply and $v_o = \mathbf{5 \text{ V}}$.



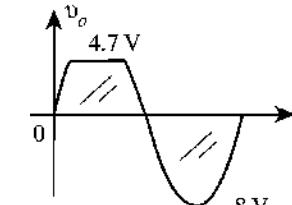35. (a) Diode “on” for $v_i \geq 4.7$ V
 For $v_i > 4.7$ V, $V_o = 4$ V + 0.7 V = **4.7 V**
 For $v_i < 4.7$ V, diode “off” and $v_o = v_i$
- (b) Again, diode “on” for $v_i \geq 3.7$ V but v_o now defined as the voltage across the diode
 For $v_i \geq 3.7$ V, $v_o = \mathbf{0.7 V}$

For $v_i < 3.7$ V, diode “off”, $I_D = I_R = 0$ mA and $V_{2.2\text{ k}\Omega} = IR = (0 \text{ mA})R = 0$ V

Therefore, $v_o = v_i - 3$ V
 At $v_i = 0$ V, $v_o = \mathbf{-3 V}$
 $v_i = -8$ V, $v_o = -8 \text{ V} - 3 \text{ V} = \mathbf{-11 V}$




36. For the positive region of v_i :
 The right Si diode is reverse-biased.
 The left Si diode is “on” for levels of v_i greater than 5.3 V + 0.7 V = 6 V. In fact, $v_o = \mathbf{6 V}$ for $v_i \geq 6$ V.

For $v_i < 6$ V both diodes are reverse-biased and $v_o = v_i$.

For the negative region of v_i :
 The left Si diode is reverse-biased.
 The right Si diode is “on” for levels of v_i more negative than 7.3 V + 0.7 V = 8 V. In fact, $v_o = \mathbf{-8 V}$ for $v_i \leq -8$ V.

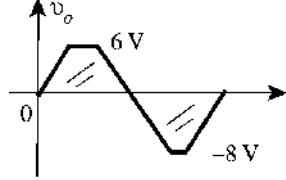For $v_i > -8$ V both diodes are reverse-biased and $v_o = v_i$.



i_R : For $-8 \text{ V} < v_i < 6 \text{ V}$ there is no conduction through the $10 \text{ k}\Omega$ resistor due to the lack of a complete circuit. Therefore, $i_R = 0$ mA.


For $v_i \geq 6$ V
 $v_R = v_i - v_o = v_i - 6 \text{ V}$
 For $v_i = 10$ V, $v_R = 10 \text{ V} - 6 \text{ V} = 4 \text{ V}$
 and $i_R = \frac{4 \text{ V}}{10 \text{ k}\Omega} = \mathbf{0.4 \text{ mA}}$

For $v_i \leq -8$ V
 $v_R = v_i - v_o = v_i + 8 \text{ V}$


For $v_i = -10 \text{ V}$

$$v_R = -10 \text{ V} + 8 \text{ V} = -2 \text{ V}$$
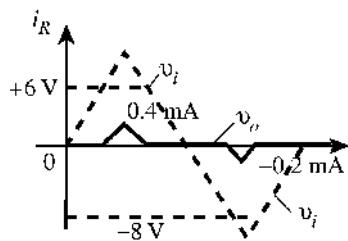
$$\text{and } i_R = \frac{-2 \text{ V}}{10 \text{ k}\Omega} = -0.2 \text{ mA}$$




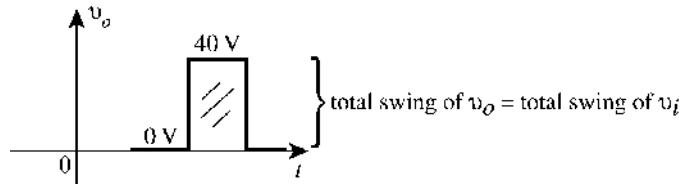37. (a) Starting with $v_i = -20 \text{ V}$, the diode is in the “on” state and the capacitor quickly charges to $-20 \text{ V}+$. During this interval of time v_o is across the “on” diode (short-current equivalent) and $v_o = 0 \text{ V}$. When v_i switches to the $+20 \text{ V}$ level the diode enters the “off” state (open-circuit equivalent) and $v_o = v_i + v_C = 20 \text{ V} + 20 \text{ V} = +40 \text{ V}$




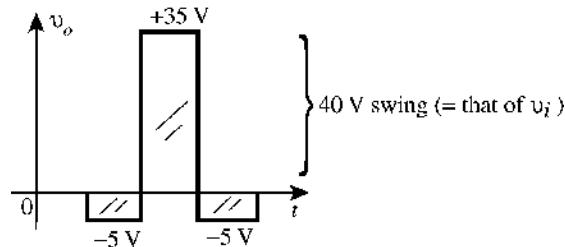- (b) Starting with $v_i = -20 \text{ V}$, the diode is in the “on” state and the capacitor quickly charges up to $-15 \text{ V}+$. Note that $v_i = +20 \text{ V}$ and the 5 V supply are additive across the capacitor. During this time interval v_o is across “on” diode and 5 V supply and $v_o = -5 \text{ V}$.


When v_i switches to the $+20 \text{ V}$ level the diode enters the “off” state and $v_o = v_i + v_C = 20 \text{ V} + 15 \text{ V} = 35 \text{ V}$.



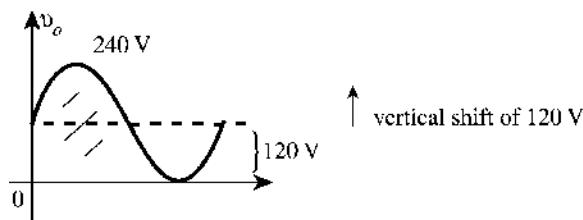38. (a) For negative half cycle capacitor charges to peak value of $120 \text{ V} = 120 \text{ V}$ with polarity $(- \text{---} (+))$. The output v_o is directly across the “on” diode resulting in $v_o = 0 \text{ V}$ as a negative peak value.
 For next positive half cycle $v_o = v_i + 120 \text{ V}$ with peak value of $v_o = 120 \text{ V} + 120 \text{ V} = 240 \text{ V}$.



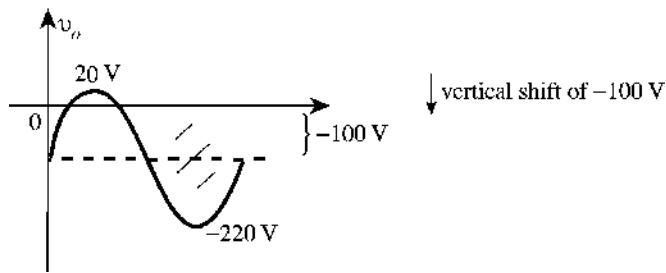- (b) For positive half cycle capacitor charges to peak value of $120 \text{ V} - 20 \text{ V} = 100 \text{ V}$ with polarity $(+ \text{---} (-))$. The output $v_o = 20 \text{ V} = 20 \text{ V}$
 For next negative half cycle $v_o = v_i - 100 \text{ V}$ with negative peak value of $v_o = -120 \text{ V} - 100 \text{ V} = -220 \text{ V}$.




39. (a) $\tau = RC = (56 \text{ k}\Omega)(0.1 \mu\text{F}) = 5.6 \text{ ms}$
 $5\tau = 28 \text{ ms}$

$$(b) 5\tau = 28 \text{ ms} \gg \frac{T}{2} = \frac{1 \text{ ms}}{2} = 0.5 \text{ ms}, 56:1$$

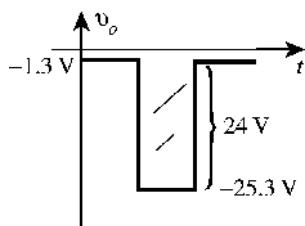
- (c) Positive pulse of v_i :
 Diode “on” and $v_o = -2 \text{ V} + 0.7 \text{ V} = -1.3 \text{ V}$
 Capacitor charges to $12 \text{ V} + 2 \text{ V} - 0.7 \text{ V} = 13.3 \text{ V}$

Negative pulse of v_i :
 Diode “off” and $v_o = -12 \text{ V} - 13.3 \text{ V} = -25.3 \text{ V}$



40. Solution is network of Fig. 2.181(b) using a 10 V supply in place of the 5 V source.

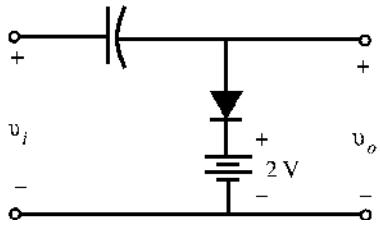41. Network of Fig. 2.178 with 2 V battery reversed.



42. (a) In the absence of the Zener diode

$$V_L = \frac{180\Omega(20\text{ V})}{180\Omega + 220\Omega} = 9\text{ V}$$

$V_L = 9\text{ V} < V_Z = 10\text{ V}$ and diode non-conducting

$$\text{Therefore, } I_L = I_R = \frac{20\text{ V}}{220\Omega + 180\Omega} = 50\text{ mA}$$

with $I_Z = 0\text{ mA}$

and $V_L = 9\text{ V}$

- (b) In the absence of the Zener diode

$$V_L = \frac{470\Omega(20\text{ V})}{470\Omega + 220\Omega} = 13.62\text{ V}$$

$V_L = 13.62\text{ V} > V_Z = 10\text{ V}$ and Zener diode “on”

Therefore, $V_L = 10\text{ V}$ and $V_{R_s} = 10\text{ V}$

$$I_{R_s} = V_{R_s} / R_s = 10\text{ V}/220\Omega = 45.45\text{ mA}$$

$$I_L = V_L/R_L = 10\text{ V}/470\Omega = 21.28\text{ mA}$$

$$\text{and } I_Z = I_{R_s} - I_L = 45.45\text{ mA} - 21.28\text{ mA} = 24.17\text{ mA}$$

- (c) $P_{Z_{\max}} = 400\text{ mW} = V_Z I_Z = (10\text{ V})(I_Z)$

$$I_Z = \frac{400\text{ mW}}{10\text{ V}} = 40\text{ mA}$$

$$I_{L_{\min}} = I_{R_s} - I_{Z_{\max}} = 45.45\text{ mA} - 40\text{ mA} = 5.45\text{ mA}$$

$$R_L = \frac{V_L}{I_{L_{\min}}} = \frac{10\text{ V}}{5.45\text{ mA}} = 1,834.86\Omega$$

Large R_L reduces I_L and forces more of I_{R_s} to pass through Zener diode.

- (d) In the absence of the Zener diode

$$V_L = 10\text{ V} = \frac{R_L(20\text{ V})}{R_L + 220\Omega}$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200$$

$$R_L = 220\Omega$$

43. (a) $V_Z = 12 \text{ V}$, $R_L = \frac{V_L}{I_L} = \frac{12 \text{ V}}{200 \text{ mA}} = 60 \Omega$

$$V_L = V_Z = 12 \text{ V} = \frac{R_L V_i}{R_L + R_s} = \frac{60 \Omega (16 \text{ V})}{60 \Omega + R_s}$$

$$720 + 12R_s = 960$$

$$12R_s = 240$$

$$R_s = 20 \Omega$$

(b) $P_{Z_{\max}} = V_Z I_{Z_{\max}}$
 $= (12 \text{ V})(200 \text{ mA})$
 $= 2.4 \text{ W}$

44. Since $I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$ is fixed in magnitude the maximum value of I_{R_s} will occur when I_Z is a maximum. The maximum level of I_{R_s} will in turn determine the maximum permissible level of V_i .

$$I_{Z_{\max}} = \frac{P_{Z_{\max}}}{V_Z} = \frac{400 \text{ mW}}{8 \text{ V}} = 50 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{8 \text{ V}}{220 \Omega} = 36.36 \text{ mA}$$

$$I_{R_s} = I_Z + I_L = 50 \text{ mA} + 36.36 \text{ mA} = 86.36 \text{ mA}$$

$$I_{R_s} = \frac{V_i - V_Z}{R_s}$$

$$\text{or } V_i = I_{R_s} R_s + V_Z$$

$$= (86.36 \text{ mA})(91 \Omega) + 8 \text{ V} = 7.86 \text{ V} + 8 \text{ V} = 15.86 \text{ V}$$

Any value of v_i that exceeds 15.86 V will result in a current I_Z that will exceed the maximum value.

45. At 30 V we have to be sure Zener diode is “on”.

$$\therefore V_L = 20 \text{ V} = \frac{R_L V_i}{R_L + R_s} = \frac{1 \text{ k}\Omega (30 \text{ V})}{1 \text{ k}\Omega + R_s}$$

$$\text{Solving, } R_s = 0.5 \text{ k}\Omega$$

$$\text{At } 50 \text{ V, } I_{R_s} = \frac{50 \text{ V} - 20 \text{ V}}{0.5 \text{ k}\Omega} = 60 \text{ mA}, I_L = \frac{20 \text{ V}}{1 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_{ZM} = I_{R_s} - I_L = 60 \text{ mA} - 20 \text{ mA} = 40 \text{ mA}$$

46. For $v_i = +50 \text{ V}$:

Z_1 forward-biased at 0.7 V

Z_2 reverse-biased at the Zener potential and $V_{Z_2} = 10 \text{ V}$.


$$\text{Therefore, } V_o = V_{Z_1} + V_{Z_2} = 0.7 \text{ V} + 10 \text{ V} = 10.7 \text{ V}$$

For $v_i = -50$ V:


Z_1 reverse-biased at the Zener potential and $V_{Z_1} = -10$ V.

Z_2 forward-biased at -0.7 V.

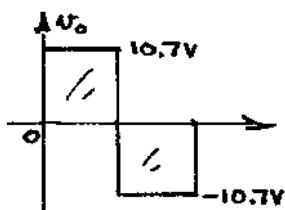Therefore, $V_o = V_{Z_1} + V_{Z_2} = \mathbf{-10.7\text{ V}}$



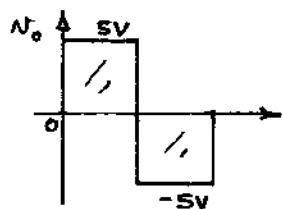For a 5 V square wave neither Zener diode will reach its Zener potential. In fact, for either polarity of v_i one Zener diode will be in an open-circuit state resulting in $v_o = v_i$.



47. $V_m = 1.414(120\text{ V}) = 169.68\text{ V}$
 $2V_m = 2(169.68\text{ V}) = \mathbf{339.36\text{ V}}$

48. The PIV for each diode is $2V_m$
 $\therefore \text{PIV} = 2(1.414)(V_{\text{rms}})$