

! This work is protected by  
US copyright laws and is for  
instructors' use only.

**Instructor's Resource Manual**  
*to accompany*

**DIGITAL ELECTRONICS**  
**A Practical Approach**

**Eighth Edition**

**William Kleitz**

*Containing*


**Solutions and Answers to In-Text Problems**  
William Kleitz, Tompkins Cortland Community College

**Solutions to Standard Logic Laboratory Manual**  
Michael Wiesner and Vance Venable

**Test Item File**  
Sohail Anwar



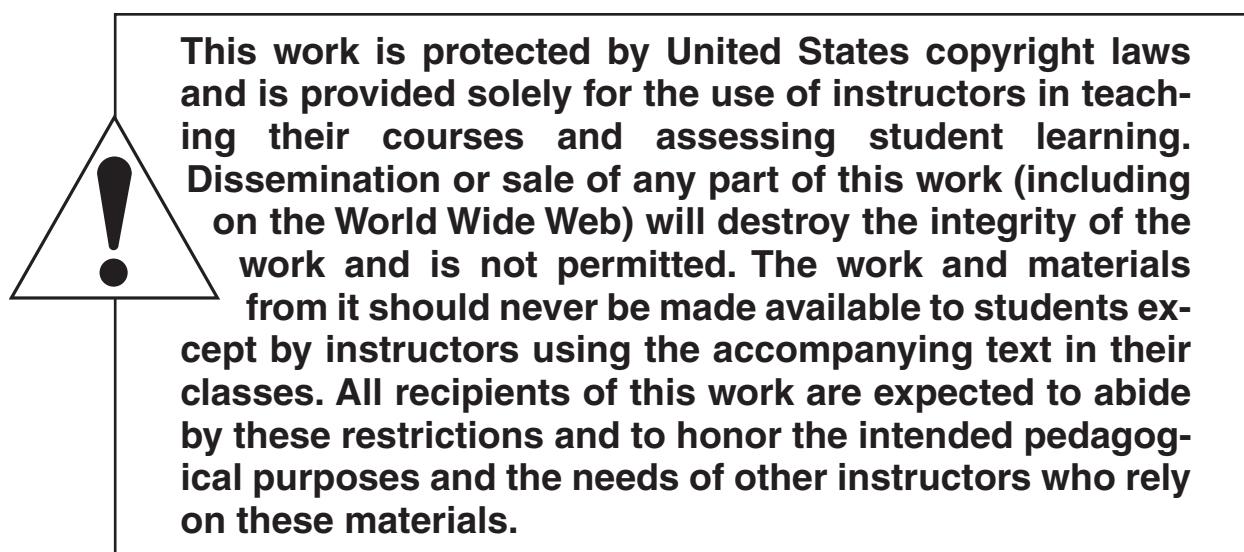Upper Saddle River, New Jersey  
Columbus, Ohio



**Copyright © 2008 by Pearson Education, Inc., Upper Saddle River, New Jersey 07458.**

Pearson Prentice Hall. All rights reserved. Printed in the United States of America. This publication is protected by Copyright and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. For information regarding permission(s), write to: Rights and Permissions Department.

**Pearson Prentice Hall™** is a trademark of Pearson Education, Inc.


**Pearson®** is a registered trademark of Pearson plc

**Prentice Hall®** is a registered trademark of Pearson Education, Inc.

Instructors of classes using Kleitz, *Digital Electronics: A Practical Approach, Eighth Edition*, may reproduce material from the instructor's resource manual for classroom use.



10 9 8 7 6 5 4 3 2 1  
ISBN-13: 978-0-13-175736-3  
ISBN-10: 0-13-175736-9

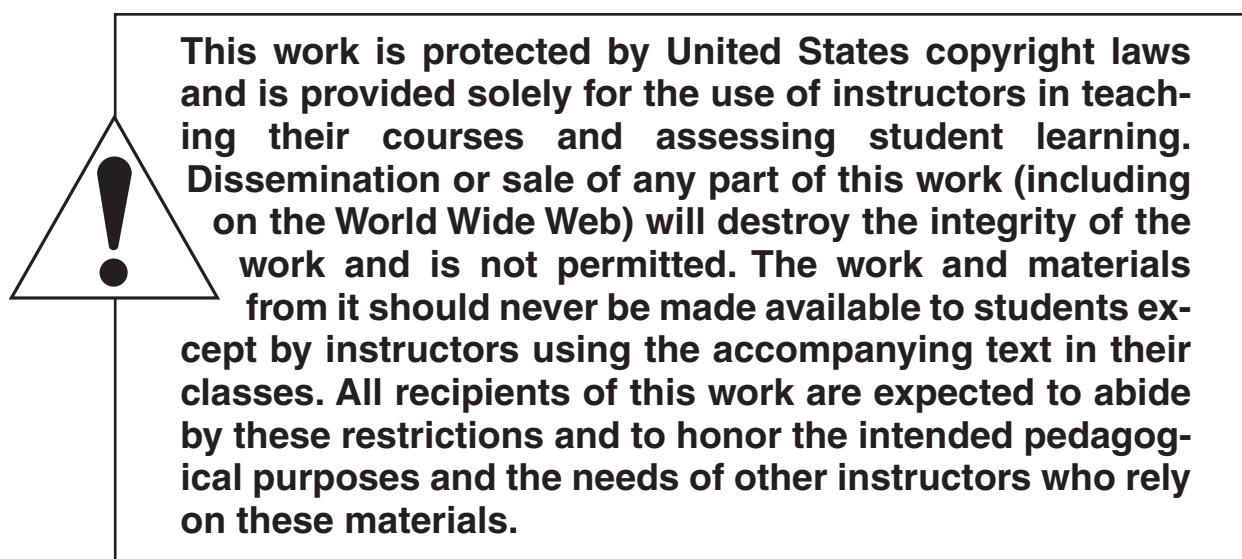**Copyright © 2008 by Pearson Education, Inc., Upper Saddle River, New Jersey 07458.**

Pearson Prentice Hall. All rights reserved. Printed in the United States of America. This publication is protected by Copyright and permission should be obtained from the publisher prior to any prohibited reproduction, storage in a retrieval system, or transmission in any form or by any means, electronic, mechanical, photocopying, recording, or likewise. For information regarding permission(s), write to: Rights and Permissions Department.

**Pearson Prentice Hall™** is a trademark of Pearson Education, Inc.

**Pearson®** is a registered trademark of Pearson plc

**Prentice Hall®** is a registered trademark of Pearson Education, Inc.

Instructors of classes using Kleitz, *Digital Electronics: A Practical Approach, Eighth Edition*, may reproduce material from the instructor's resource manual for classroom use.



10 9 8 7 6 5 4 3 2 1  
ISBN-13: 978-0-13-243579-6  
ISBN-10: 0-13-243579-9

# Preface

This *Instructor's Resource Manual* is part of the extensive package of ancillary material available to enhance the teaching and learning process. These products represent the most thorough selection of print, electronic, multimedia, and Internet tools available. This package underscores Prentice Hall's commitment to enable you to prepare and deliver readily the best content presentations and student learning and testing tools. These products very effectively complement the parent textbook, *Digital Electronics: A Practical Approach, Eighth Edition*, the best-selling work in this discipline by respected author William Kleitz.

Components in this *Instructor's Resource Manual* are:

- Solutions and Answers to In-text Problems, by William Kleitz
- Solutions to the Standard Logic *Laboratory Manual to accompany Digital Electronics* (ISBN 0-13-223982-5), by Michael Wiesner and Vance Venable.
- Test Item File containing over 1000 additional multiple-choice questions that can be used to develop weekly quizzes, tests, or final exams.

Other parts of the overall ancillary package from Prentice Hall are:

- Two CD-ROM's packaged with each copy of the parent textbook, containing:  
Selected schematics from the text rendered in Multisim 6.0, 7.0, 8.0, and 9.0.  
Solutions to in-text Altera CPLD examples  
Solutions to in-text Xilinx CPLD examples  
Texas Instruments' fixed-function data sheets

- PowerPoint slides on CD-ROM (ISBN 0-13-223981-7) containing:  
All figures from the text  
Lecture notes for all chapters  
Also available online.
- Three Laboratory Manuals
  1. Standard Logic  
*Laboratory Manual to accompany Digital Electronics*, by Michael Wiesner and Vance Venable (ISBN 0-13-223982-5)
  2. Altera CPLDs  
*Digital Logic Simulation and CPLD Programming*, by Steve Waterman (DeVry University) (ISBN 0-13-171514-3)
  3. Xilinx CPLDs  
*Digital Electronics Laboratory Experiments*, by James Stewart and Chao-Ying Wang (DeVry University) (ISBN 0-13-113124-9)
- *TestGen*, a computerized test bank for producing customized tests and quizzes (ISBN 0-13-243607-8)
- *Companion Website*, a student resource containing additional multiple-choice questions and other textbook-related links, found at <http://www.prenhall.com/kleitz>

For more information about these supplements, contact your Prentice Hall sales representative. And for more information about other new technology products, visit [www.prenhall.com](http://www.prenhall.com)



# Contents

**Solutions and Answers to In-text Problems.....1**

**Solutions to the Standard Logic Laboratory Manual.....49**

**Test Item File.....59**



# Solutions and Answers to In-text Problems

## Chapter 1



- 1–1.** (a)  $6_{10}$  (b)  $11_{10}$  (c)  $9_{10}$  (d)  $7_{10}$   
 (e)  $12_{10}$  (f)  $75_{10}$  (g)  $55_{10}$  (h)  $181_{10}$   
 (i)  $167_{10}$  (j)  $118_{10}$
- 1–2.** (a)  $1011\ 1010_2$  (b)  $1101\ 0110_2$   
 (c)  $0001\ 1011_2$  (d)  $1111\ 1011_2$   
 (e)  $1001\ 0010_2$
- 1–3.** (a)  $31_8$  (b)  $35_8$  (c)  $134_8$  (d)  $131_8$   
 (e)  $155_8$
- 1–4.** (a)  $100\ 110_2$  (b)  $111\ 100_2$  (c)  $110\ 001_2$   
 (d)  $011\ 010_2$  (e)  $101\ 111_2$
- 1–5.** (a)  $23_{10}$  (b)  $31_{10}$  (c)  $12_{10}$  (d)  $58_{10}$   
 (e)  $41_{10}$
- 1–6.** (a)  $176_8$  (b)  $61_8$  (c)  $127_8$  (d)  $136_8$   
 (e)  $154_8$
- 1–7.** (a)  $B9_{16}$  (b)  $DC_{16}$  (c)  $74_{16}$  (d)  $FB_{16}$   
 (e)  $C6_{16}$
- 1–8.** (a)  $1100\ 0101_2$  (b)  $1111\ 1010_2$   
 (c)  $1101\ 0110_2$  (d)  $1010\ 1001\ 0100_2$   
 (e)  $0110\ 0010_2$
- 1–9.** (a)  $134_{10}$  (b)  $244_{10}$  (c)  $146_{10}$   
 (d)  $171_{10}$  (e)  $965_{10}$
- 1–10.** (a)  $7F_{16}$  (b)  $44_{16}$  (c)  $6B_{16}$  (d)  $3D_{16}$   
 (e)  $1D_{16}$
- 1–11.** (a)  $98_{10}$  (b)  $69_{10}$  (c)  $74_{10}$  (d)  $36_{10}$   
 (e)  $81_{10}$
- 1–12.** (a)  $1000\ 0111_{BCD}$  (b)  $0001\ 0100\ 0010_{BCD}$   
 (c)  $1001\ 0100_{BCD}$  (d)  $0110\ 0001_{BCD}$   
 (e)  $0100\ 0100_{BCD}$

- 1–13.** (a) 010 0101  
 (b) 0100100 0110001 0110100  
 (c) 1001110 0101101 0110110  
 (d) 1000011 1010000 1010101  
 (e) 1010000 1100111
- 1–14.** (a) 25 (b) 243134 (c) 4E2D36  
 (d) 435055 (e) 5067
- 1–15.** (a) Tank A, temperature high; tank C, pressure high  
 (b) Tank D, temperature and pressure high  
 (c) Tanks B and D, pressure high  
 (d) Tanks B and C, temperature high  
 (e) Tank C, temperature and pressure high
- 1–16.** 0001 0010 0000<sub>BCD</sub>
- 1–17.** (a) sku43 (b) 534B553433<sub>16</sub>
- 1–18.** (a) 68HC11EMFN, C3 (b) 27C64, A8  
 (c) 2N3904, F4 (d) DB9, E1
- 1–19.** 16-MAR 1995 Revision A
- 1–20.** (a) 2 (b) 2 (c) 4 (d) 1
- E1–1.** (a) 0000 0101  
 (b) Eleven  
 (c) 0E  
 (d) 27
- E1–2.** (a) 40  
 (b) 55  
 (c) Tank B pressure and temperature are HIGH.  
 (d) All pressures are HIGH.

## Chapter 2

- 2-1.** (a)  $t_p = 1/2 \text{ MHz} = 0.5 \mu\text{s}$   
 (b)  $t_p = 1/500 \text{ kHz} = 2 \mu\text{s}$   
 (c)  $t_p = 1/4.27 \text{ MHz} = 0.234 \mu\text{s}$   
 (d)  $t_p = 1/17 \text{ MHz} = 58.8 \text{ ns}$   
 (e)  $f = 1/2 \mu\text{s} = 500 \text{ kHz}$   
 (f)  $f = 1/100 \mu\text{s} = 10 \text{ kHz}$   
 (g)  $f = 1/0.75 \text{ ms} = 1.33 \text{ kHz}$   
 (h)  $f = 1/1.5 \mu\text{s} = 0.667 \text{ MHz}$


- 2-2.** (a)

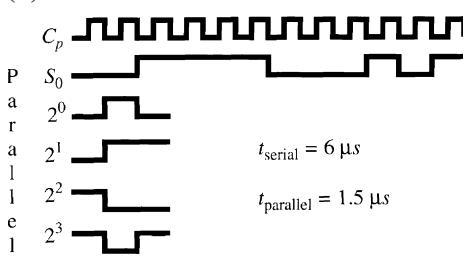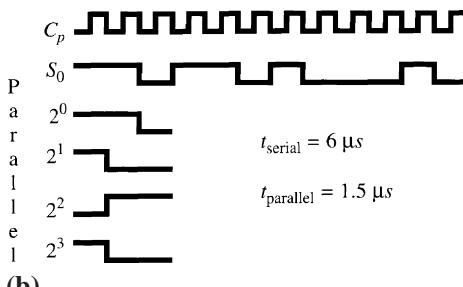

- 2-3.** (a)  $8 \times (1/3.7 \text{ MHz}) = 2.16 \mu\text{s}$   
 (b)  $1.21 \mu\text{s}$  occurs during the 5th period which is LOW.

- 2-4.** (a)  $3 \times (1/8 \text{ MHz}) = 0.375 \mu\text{s}$   
 (b)  $6 \times (1/4.17 \text{ MHz}) = 1.44 \mu\text{s}$

- 2-5.**

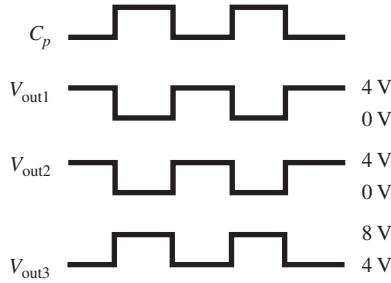

- 2-6.** D<sub>1</sub> = REV      D<sub>8</sub> = REV  
 D<sub>2</sub> = FOR      D<sub>9</sub> = REV  
 D<sub>3</sub> = FOR      D<sub>10</sub> = REV  
 D<sub>4</sub> = REV      D<sub>11</sub> = REV  
 D<sub>5</sub> = REV      D<sub>12</sub> = REV  
 D<sub>6</sub> = REV      D<sub>13</sub> = REV  
 D<sub>7</sub> = FOR


- 2-7.** V<sub>1</sub> = 0 V      V<sub>5</sub> = 4.3 V  
 V<sub>2</sub> = 4.3 V      V<sub>6</sub> = 5.0 V  
 V<sub>3</sub> = 4.3 V      V<sub>7</sub> = 0 V  
 V<sub>4</sub> = 0 V

- 2-8.** That diode will conduct, lowering V<sub>6</sub> to 0.7 V ("AND").

- 2-9.** That diode will conduct, raising V<sub>7</sub> to 4.3 V ("OR").

- 2-10.** V<sub>out1</sub> ≈ 0 V, V<sub>out2</sub> ≈ 5 V

- 2-11.**

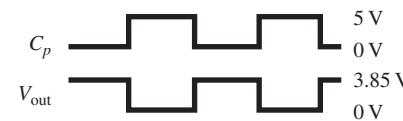

- 2-12.** Input signal to BASE (B); output signal from COLLECTOR (C).

- 2-13.** The transistor is cutoff;

$$V_{out} = 5 \text{ V} \times 1 \text{ M}\Omega / (330 \text{ }\Omega + 1 \text{ M}\Omega)$$

$$V_{out} = 4.998 \text{ V}$$


- 2-14.** V<sub>out</sub> is lowered with a smaller load resistor;  
 $V_{out} = 5 \text{ V} \times 470 \text{ }\Omega / (330 \text{ }\Omega + 470 \text{ }\Omega)$   
 $V_{out} = 2.94 \text{ V}$

- 2-15.** Because, when the transistor is turned on (saturated), the collector current will be excessive ( $I_C = 5 \text{ V}/R_C$ ).

- 2-16.**  $I_C = 5 \text{ V}/100 \text{ }\Omega = 50 \text{ mA}$

- 2-17.** The totem-pole output replaces  $R_C$  with a transistor that acts like a variable resistor. The transistor prevents excessive collector current when it is cut off and provides a high-level output when turned on.

- 2-18.**

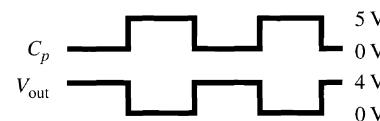

- 2-19.** (a) 8.0 MHz (b) 125 ns

- 2-20.** (a) 9.8304 MHz (b) 101.73 ns

- 2-21.** P3 parallel, P2 serial

- 2-22.** reverse

- 2-23.** A HIGH on pin 2 will turn Q1 on, making RESET\_B approximately zero.

- E2-1.** (a) Let

- (b) 24

- E2-2.** (a) Sit  
 (b) 3

- E2-3.** (a) Cp = 5V/0V, Vout3 = 0V/5V  
 inverse of each other

- (b) Cp = 5V/0V, Vout3 = 0V/8V

- (c) Cp and Vout3 are in phase.

**E2-4.** (a)  $C_p = 5V/0V$ ,  $V_{out3} = 10V/6V$ , in phase

(b)  $C_p = 5V/0V$ ,  $V_{out3} = 10V/8V$

(c) it would be inverted.

**E2-5.** (a)  $V1 = 4.3V$ ,  $V2 = 0V$ ,  $V3 = 4.3V$ ,  $V4 = 0.7V$

(b)  $V1 = 0V$ ,  $V2 = 4.3V$ ,  $V3 = 0V$ ,  $V4 = 5.0V$  (Both diodes are reverse biased.)

**E2-6.** (a)  $C_p = 5V/0V$ ,  $V_{out} = 0V/5V$ , inverse of each other

(b)  $C_p = 5V/0V$ ,  $V_{out} = 0V/8V$

### Chapter 3

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

**3-2.**  $2^8 = 256$

**3-3.** (a) The output is HIGH whenever all inputs are HIGH; otherwise, the output is LOW.

(b) The output is HIGH whenever any input is HIGH; otherwise, the output is LOW.

**3-4.**  $W = 0, X = 1, Y = 0, Z = 0$


**3-5.**  $X = ABC$

$X = ABCD$


$X = A + B + C$

**3-6.**  $W = 1, X = 0, Y = 1, Z = 1$


**3-7.**

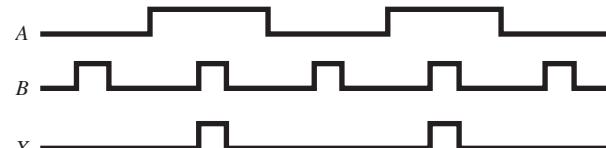


**3-8.**






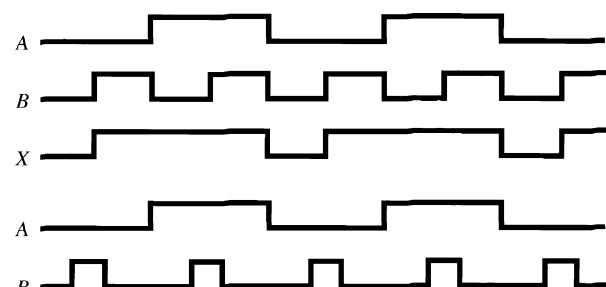


**3-9.**


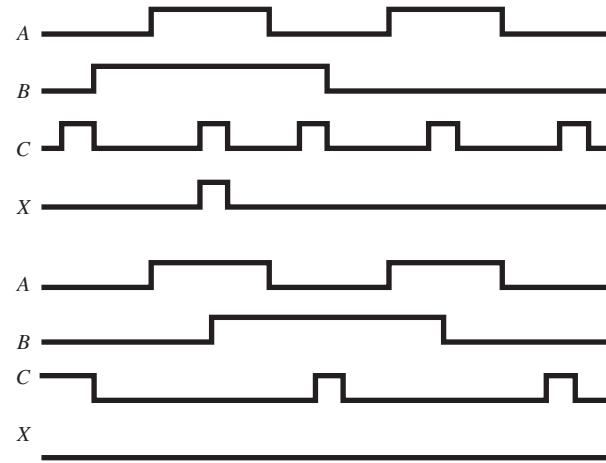


**3-10.**

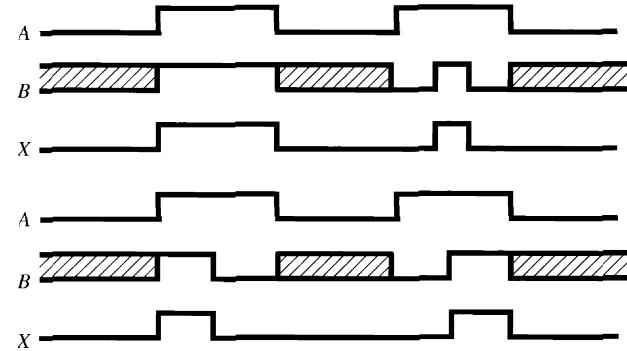

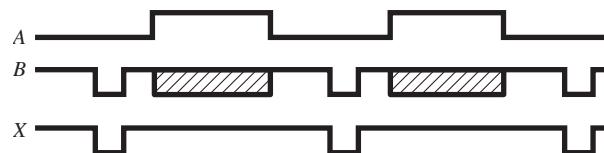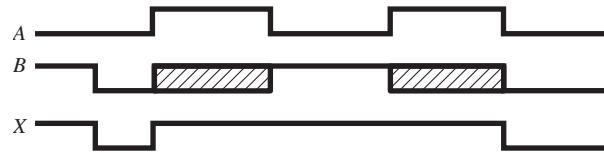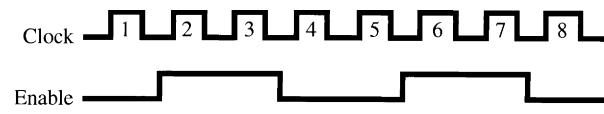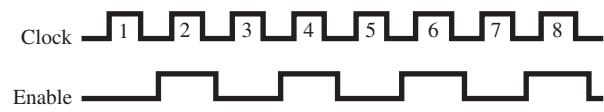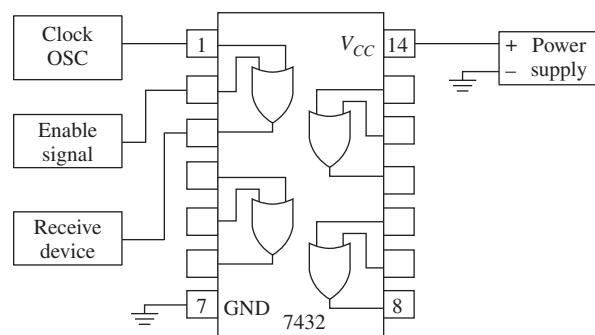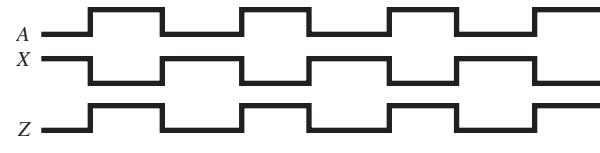**3-11.****3-12.****3-13.****3-14.** Four**3-15.****3-16.** Four**3-17.** Two**3-18.** HIGH, LOW, and FLOAT**3-19.** To provide pulses to a digital circuit for troubleshooting purposes.**3-20.** LOW, to enable the output to change with pulser (if gate is good).**3-21.** HIGH, to enable the output to change with pulser (if gate is good).**3-22.** Pin 3 should be flashing; the AND gate is bad.**3-23.** Pin 2 should be ON; the Enable switch is bad, or bad Enable connection.**3-24.** Pin 3 should be flashing and pin 7 should be OFF. There is a bad ground connection to pin 7.**3-25.**  $X = \bar{A}, X = 0$ **3-26.**  $X = \bar{A}, Z = A, X = 1, Z = 0$ **3-27.****3-28.**  $X = \overline{AB}, Y = \overline{CD}$ 


A	B	X	C	D	Y
0	0	1	0	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	1	1	0

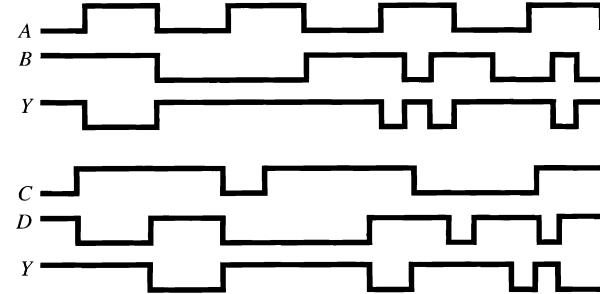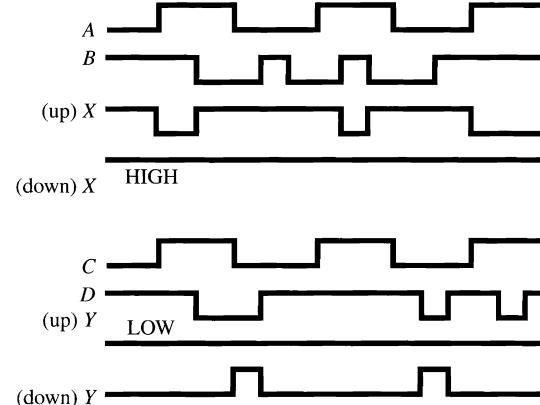**3-29.**  $W = 1$  $X = 1$  $Y = 1$  $Z = 0$ **3-30.****3-31.**  $W = 1$  $X = 0$  $Y = 0$  $Z = 0$ **3-32.****3-33.** It disables the other two inputs when it is DOWN for the NAND and UP for the NOR.


**3-34.**  $X = \overline{A} + B + \overline{C}$     $Y = \overline{D} + \overline{E} + F$

A	B	C	X	D	E	F	Y
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	0
1	0	0	0	1	0	0	0
1	0	1	0	1	0	1	0
1	1	0	0	1	1	0	0
1	1	1	0	1	1	1	0


**3-35.**

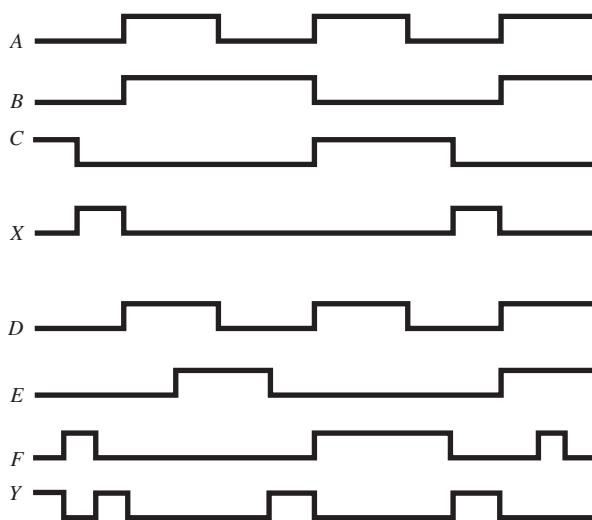

**3-36.**

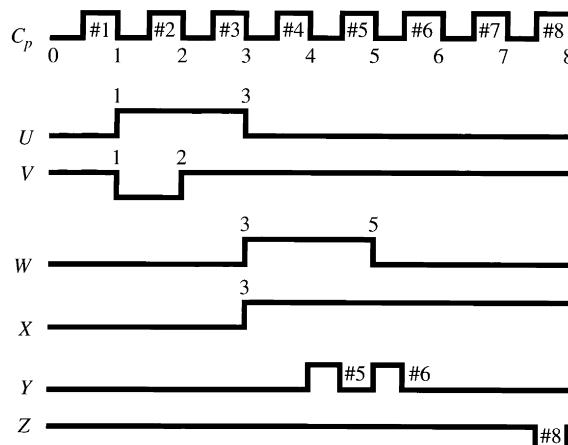


**3-37.**

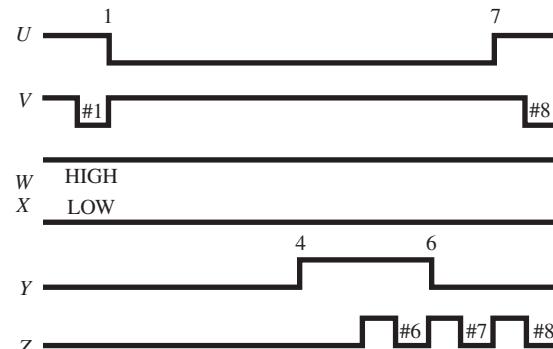


- 3-38.** (a)  $\overline{A}C$    (b)  $CD$    (c)  $\overline{A}CD$    (d)  $C_P\overline{A}\overline{B}$   
 (e)  $AC$    (f)  $C_PAB$

**3-39.**  $U = C_PAB$     $W = BC$   
 $V = \overline{C}D$     $X = C_PCD$

**3-40.**

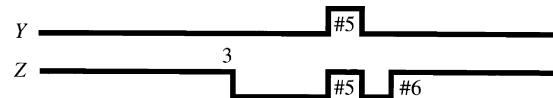

**3-41.**

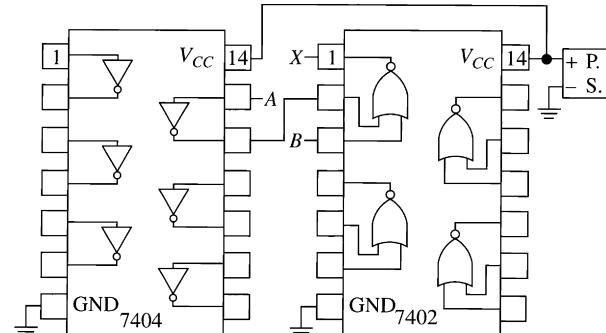

**3-42.** LOW; to see inverted output pulses (otherwise, output would always be LOW).

**3-43.** HIGH; to see inverted output pulses (otherwise, output would always be HIGH).

**3-44.** Pins 4 and 10 should be HIGH. The inverters connected to those pins are bad.

**3-45.** There is no problem.

**3-46.** The inverter is not working.

**3-47.** With all inputs HIGH, pin 8 should be LOW. Next try making each of the 8 inputs LOW, one at a time, while checking for a HIGH at pin 8.

**3-48.** Pins 8 and 12 should be LOW. The NORs connected to those pins are bad.

**3-49.** AND - 74HC08; U3:A = location C2, U3:B = location D2 OR - 74HC32; location B7

**3-50.** (a) flashing   (b) HIGH

**3-51.** pin 20 = LOW (GND), pin 40 HIGH (+5)

**3–52.** Because they are all part of one IC package.

**3–53.** Place probe “A” on the input of the inverter (WATCHDOG\_CLK). Using the same settings for probe “B” as “A,” place probe “B” on the output of U4:A. “B” should be the complement of “A.”

**3–54.** all HIGH

**3–55.** OE\_B

**E3–1.** (a)  $X = 1, Y = 1$

(b)  $X = 0, Y = 0$

(c)

A	B	X	A	B	Y
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1

**E3–2.** (a) AND

(b) OR

**E3–3.** (a) Up

(b) Down

**E3–4.** Up ('1')

**E3–5.** (a) Vcc

(b) Logic pulser

(c) Logic probe

(d) Ground

(e) Vcc

**E3–6.** Password for Options-Circuit Restrictions  
Hide component faults is: **wk5e**

(a) Gates 2 and 3

(b) Gate 3

(c) Gates 1 and 4

**E3–7.** (a)  $X = 0, Y = 0$

(b)  $X = 1, Y = 1$

(c)

A	B	X	A	B	Y
0	0	1	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0

**E3–8.** (a) NOR

(b) NAND

**E3–9.** (a) Yes

(b)  $X = AB$

(c) 6mS

**E3–10.** (a)  $T_1 = 6\text{mS}, T_2 = 10\text{mS}$ ,  
 $T_2 - T_1 = 4\text{mS}$

(b) Two

(c) 1mS

**E3–11.** (a) NAND

(b) NOR

**E3–12.** (a) OR

(b) NAND

**E3–13.** (a)  $X = C', D', \text{Cp}$

(b)  $Y = BD'$

**E3–14.** Password for Options-Circuit Restrictions-  
Hide component faults is: **wk5e**

(a) U1b, U1c, are bad

(b) U2c, U2d are bad

**E3–15.** Password for Options-Circuit Restrictions-  
Hide component faults is: **wk5e**

(a) U1b, U1c, U1d are bad

(b) U2a, U2c are bad

**E3–16.** Password for Options-Circuit Restrictions-  
Hide component faults is: **wk5e**

(a) U1a, U1c are bad

(b) U2c, U2d are bad

**E3–17.** Password for Options-Circuit Restrictions-  
Hide component faults is: **wk5e**

(a) U1b, U1c are bad

(b) U2a, U2d are bad

## Chapter 4

**4–1.** The 7400-series uses hard-wired logic. The designer must use a different IC for each logic function. Programmable logic contains thousands of logic gates that can be custom-configured by the designer to perform any logic desired.

**4–2.** Schematic capture using a CAD system or a Hardware Description Language like VHDL.

**4–3.** Hardware Description Language

**4–4.** (1) Define the problem, (2) develop the equations, (3) enter the design, (4) simulate the I/O conditions, (5) program the PLD, (6) test the PLD with actual I/O.

**4–5.** (a) 3, (b) 5

**4–6.** A small indented circle



**4–7.** They receive programming information from a PC and program the on-board CPLD that can then be tested with actual I/O signals.

**4–8.** (a) 3

(b) 2

(c) 3

**4–9.** The PLA provides programmable OR gates for combining the product terms.

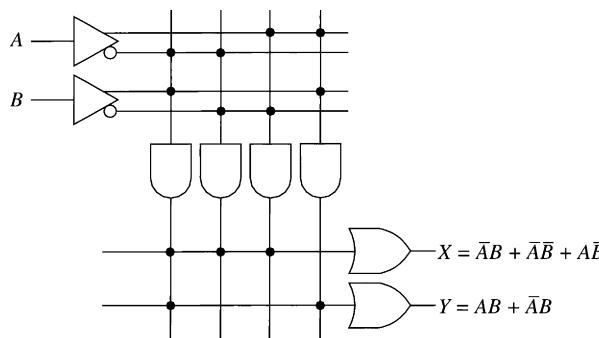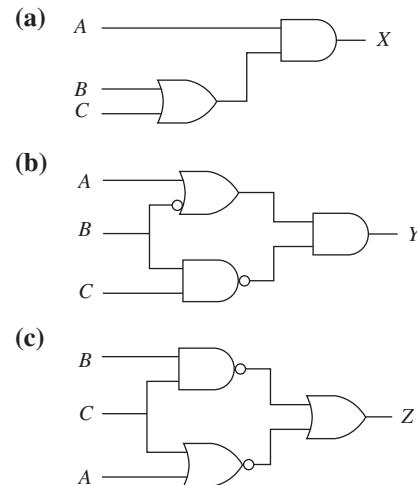**4-10.****4-23.**

**4-11.** So that it won't lose its programmed logic design when power is removed.

**4-12.** (a) 2500 usable gates, 128 macrocells  
(b) 2400 usable gates, 108 macrocells

**4-13.** The look-up table method

**4-14.** Inputs      Output

A	B	X
0	0	1
0	1	0
1	0	1
1	1	0

- 4-15.** They must be re-programmed.  
**4-16.** Schematic entry using a CAD system and VHDL entry using a text editor.  
**4-17.** It translates the information from the design entry stage into a binary file that is later used to program the CPLD.  
**4-18.** It defines the IC pin as an input or output and connects it to the internal CPLD circuitry.  
**4-19.** Text  
**4-20.** (a) Library declares which VHDL library to use.  
(b) Entity defines the input/output ports.  
(c) Architecture defines the logic expressions.

**4-21.** ENTITY and3 IS  
PORT(

    A, B, C: IN bit;  
    X :OUT bit);

END and3;


**4-22.** ARCHITECTURE arc OF and3 IS  
BEGIN  
    X<=(A AND B AND C);  
END arc;


## Chapter 5

$$\begin{aligned}5-1. \quad W &= (A + B)(C + D) \\ X &= AB + BC \\ Y &= (AB + B)C \\ Z &= (AB + B + (B + C))D\end{aligned}$$

- 5-2.** (a)  $R = TPF$   
(b)  $G = TP(M + F)$   
(c)  $B = F(H + T + P)$

**5-3.**

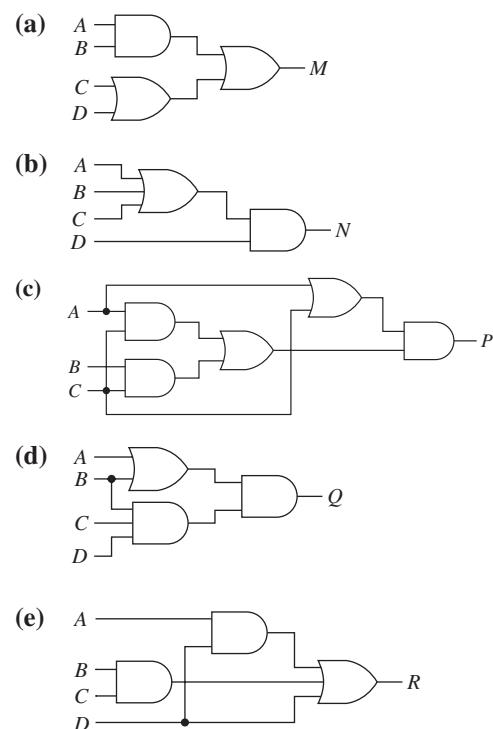


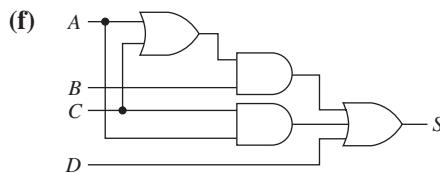

A	B	C	D	M	N	Q	R	S
0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	1	1
0	0	1	0	1	0	0	0	0
0	0	1	1	1	1	0	1	1
0	1	0	0	0	0	0	0	0
0	1	0	1	1	1	0	1	1
0	1	1	0	1	0	0	1	1
0	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1	1
1	0	1	0	1	0	0	0	1
1	0	1	1	1	1	0	1	1
1	1	0	0	1	0	0	0	1
1	1	0	1	1	1	0	1	1
1	1	1	0	1	0	0	1	1
1	1	1	1	1	1	1	1	1

A	B	C	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

5-4.

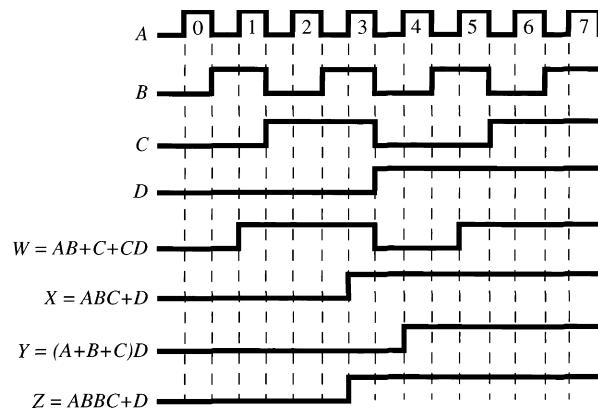

5-5. (a) Commutative law (b) Associative law  
(c) Distributive law

5-6.  $M = O$

$N = 1$

$P = AB$

$Q = C + D$

$R = A$

$S = 0$

$T = A$

$U = 1$

$V = A$

$W = A$

5-7.

$$W = (A + B)BC$$

$$W = BC$$

$$X = (A + B)(B + C)$$



$$X = B + AC$$

$$Y = A + (A + B)BC$$

$$Y = A + BC$$

$$Z = AB + B + BC$$

$$Z = B$$

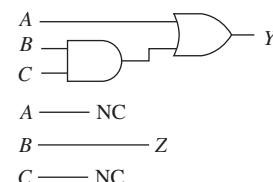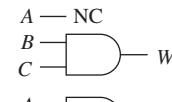

5-8.

$$X = (A + B)(B + C) + B + C$$


$$X = B + C$$

$$Y = (A + B)(B + C)A$$




$$Y = A(B + C)$$


$$Z = AB + AB(B + C)$$

$$Z = AB$$

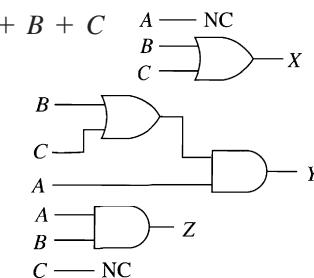


5-9.

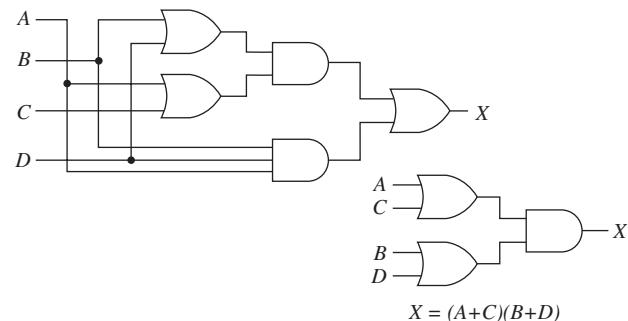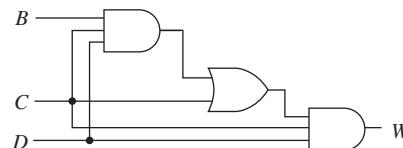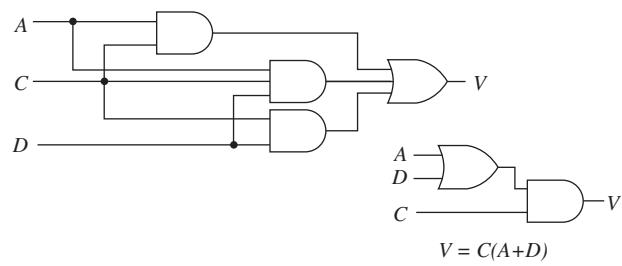

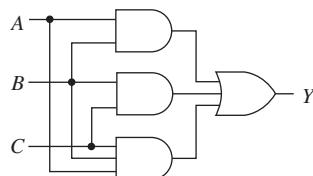

$$Y = (A+C)B$$

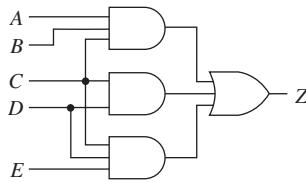

$$Z = ABC + CD$$


**5-10.**

A	C	D	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

A	B	C	D	X	Z	C	D	W
				0	0			
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	0	0
0	0	1	1	1	1	1	1	1
0	1	0	0	0	0			
0	1	0	1	0	0			
0	1	1	0	1	0			
0	1	1	1	1	1			
1	0	0	0	0	0			
1	0	0	1	1	0			
1	0	1	0	0	0			
1	0	1	1	1	1			
1	1	0	0	1	0			
1	1	0	1	1	0			
1	1	1	0	1	1			
1	1	1	1	1	1			

$$5-11. X = (A + B)(D + C)$$

$$5-12. Y = B(AC + D)$$

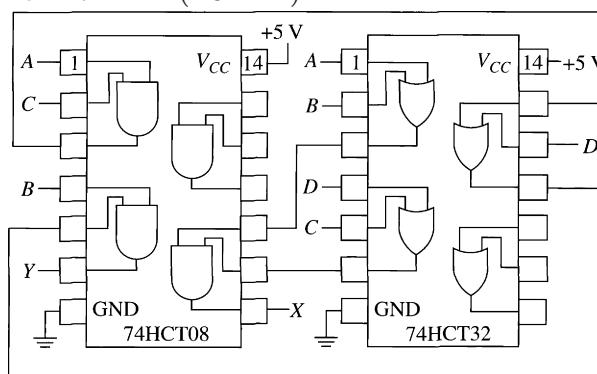


**5-13.** Break the long bar and change the AND to an OR, or the OR to an AND.

**5-14. (a) NAND (b) NOR**


**5-15.**  $Y$  and  $Z$  are both ORs.

$$5-16. \overline{A} + \overline{B} = \overline{\overline{A}} \overline{\overline{B}} = AB$$


**5-17.**

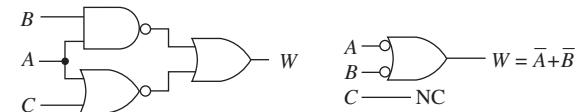


$$W = \overline{A} + \overline{B}$$

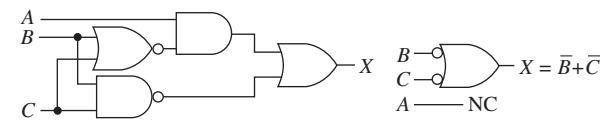

$$X = \overline{B} + \overline{C}$$

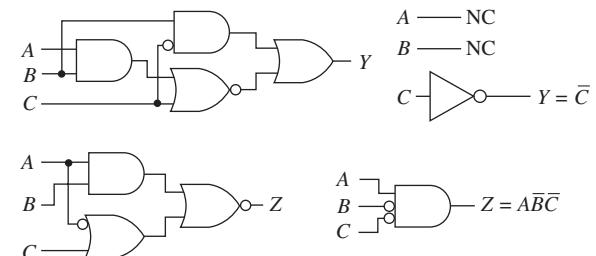

$$Y = \overline{C}$$

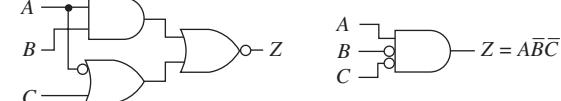

$$Z = A\overline{B}\overline{C}$$


$$5-18. (a) X = \overline{AB} + (B + C)$$

$$X = 0$$


$$(b) Y = \overline{A} + BBC$$

$$Y = 1$$




**5-19.**

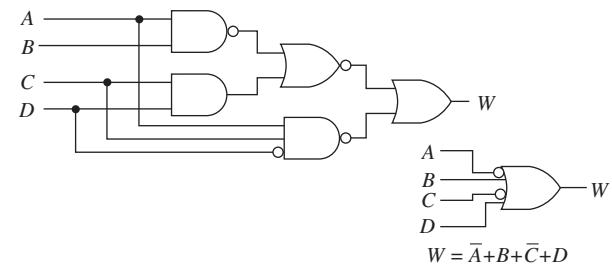
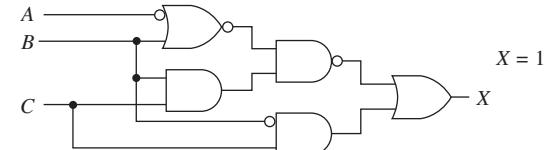
$$W = \overline{A} + \overline{B} + \overline{C} + D$$



$$X = 1$$

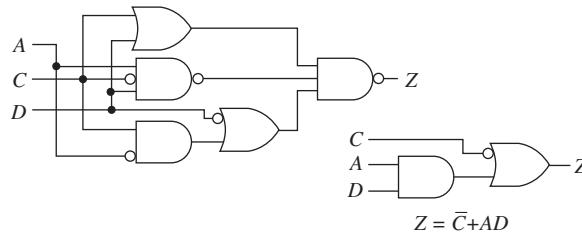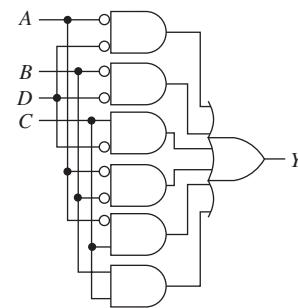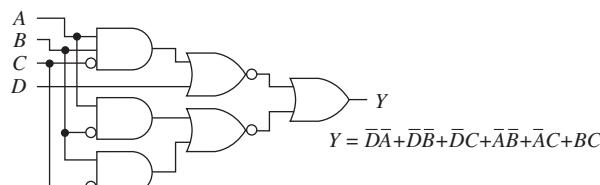


**5-20. (a)**  $X = (\overline{A} + \overline{B}) + \overline{BC} + \overline{BCD}$


$$X = ABC + \overline{BD} + \overline{CD}$$

**(b)**  $Y = \overline{AB} + \overline{ABC} \cdot (\overline{B} + \overline{C})$


$$Y = 1$$

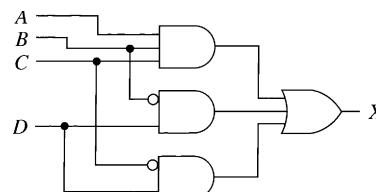


**5-21.**

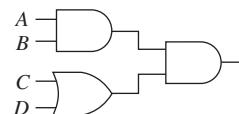

**5-22.**

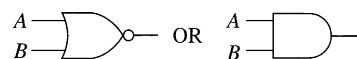

**5-23.**

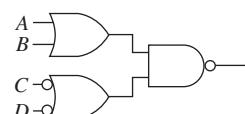

**5-24.**

**5-25.**

- (2<sup>3</sup>) A ————— AND ————— ABCD>11
- (2<sup>2</sup>) B ————— AND ————— NC
- (2<sup>1</sup>) C ————— NC
- (2<sup>0</sup>) D ————— NC

**5-26.**


- (2<sup>3</sup>) A ————— AND ————— ABCD>7 and <10
- (2<sup>2</sup>) B ————— NOT ————— NC
- (2<sup>1</sup>) C ————— NOT ————— NC
- (2<sup>0</sup>) D ————— NC

**5-27.**

A	B	C	W	X
0	0	0	0	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	0


A	B	C	D	Y	Z
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	0	1
0	1	0	1	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

**5-28.**

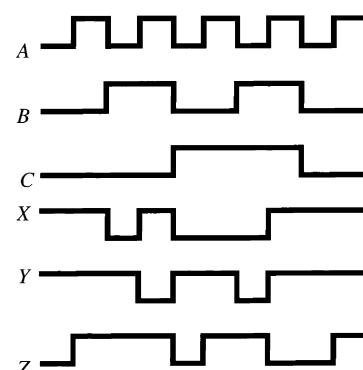

**5-29.**

- (a) ————— AND —————
- (b) ————— AND —————
- (c) ————— AND —————
- (d) ————— AND —————

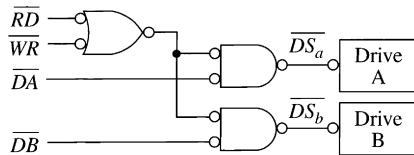**5-30.****5-31.**

(a)  $A \rightarrow X = \bar{A}$

(b)  $A \rightarrow X = \bar{A}$

**5-32.**

(a)  $A, B \rightarrow X = A+B$

(b)  $A, B \rightarrow X = AB$

(c)  $A, B \rightarrow X = AB$



(d)  $A, B \rightarrow X = \overline{A+B}$

**5-33.**



(a)  $A, B, C \rightarrow X$

(b)  $A, B, C \rightarrow X$  with a 'CANCEL' input that bypasses the first AND gate.

(c)  $A, B, C \rightarrow X$

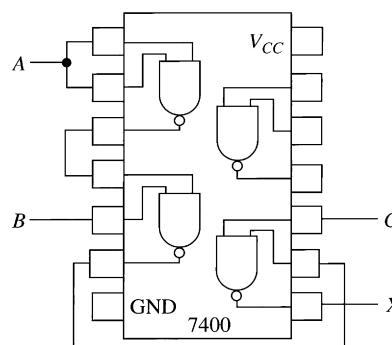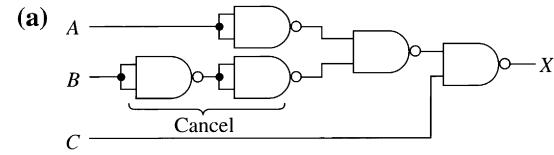**5-34.**

(b)

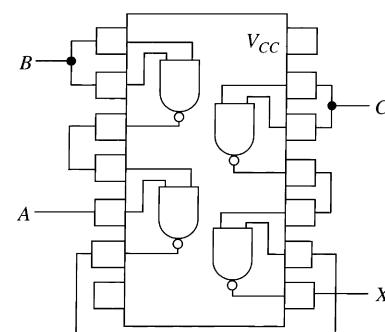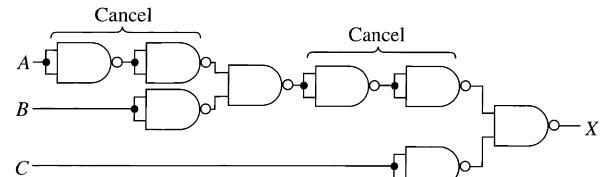**5-35.** u. SOP


v. POS

w. POS

x. SOP

y. POS

z. POS, SOP

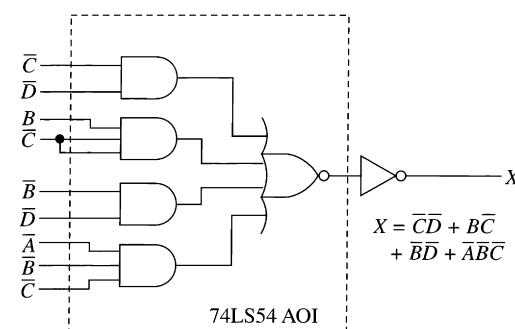**5-36.**

**5-37.**  $X = \bar{A} + B\bar{C}$

$Y = B + \bar{A}C$

$Z = A\bar{C} + AB + \bar{A}\bar{B}C$

**5-38.**  $W = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}\bar{B}$

$X = \bar{C}\bar{D} + \bar{B}\bar{D} + ABCD$


$Y = A\bar{B} + A\bar{D} + \bar{B}\bar{C}\bar{D}$

$Z = \bar{C} + \bar{B}\bar{D} + \bar{A}\bar{D}$

**5-39.** (a)  $X = \bar{C}D + AC + B$


(b)  $Y = 1$

**5-40.**

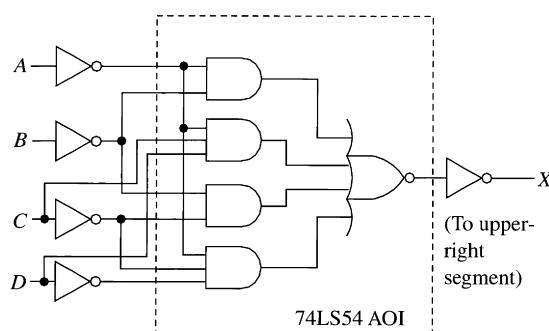

$$X = \bar{A}\bar{B} + \bar{A}CD + \bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} \text{ where } A = \text{MSB}$$

**5-41.**

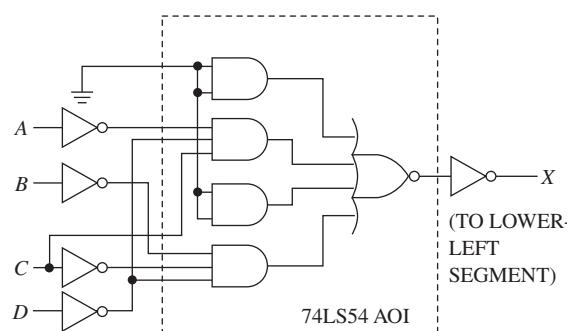

$$X = \bar{A}\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \text{ where } A = \text{MSB}$$

**5-42.** Pin 6 should be ON; bad gate.

**5-43.** The IC checks out OK. The problem is that pin 9 should be connected to pin 10 (not 9 to GND).

**5-44.** The output (pin 8) would be stuck high.

**5-45.** WATCHDOG\_EN · Qa

**5-46.** WATCHDOG\_EN · Qa + Qb

**5-47.** (a) pin 6 = P1.0 + A15 (b) AND

(c) quad 2 input AND

(d) RD is LOW or WR is LOW

**5-48.** Pin 20 of U10 goes LOW if RESET and A15 are both LOW.

**E5-1.** (a)  $B = KD + HD$

(b)  $B = D(K + H)$

**E5-2.** (a) Seven

(b)  $X = AB + BC$

**E5-3.** (a) 5

(b)  $X = BC + A$

**E5-4.** (a)  $X = (A + B)(B + C) + (B + C)$


(b) Six

(c)  $X = B + C$

**E5-5.** (a) 2

(b)  $X = BC$


(c)

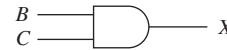

**E5-6.** (a) Ten

(b)  $X = ABD + CD$

(c)

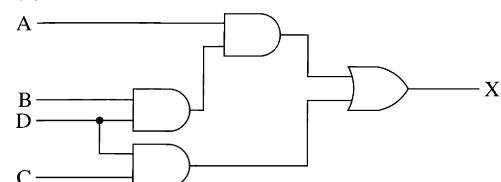

$$\text{E5-7. } X = AB'C' + A'BC' + AB'C$$

$$\text{E5-8. } X = A'BC' + AB'C + A'BC + ABC$$

**E5-9.** (a) 2

(b)  $X = B'C'$

**E5-10.** (a)  $X = ((A + B)'(B + C))'$

(b) 7

(c)  $X = A + C' + B$

**E5-11.** (a) 6

(b)  $X = B' + C'$


(c)






**E5-12.** (a) 11

(b)  $X = A'B' + A'D' + B'D' + BC$

(c)

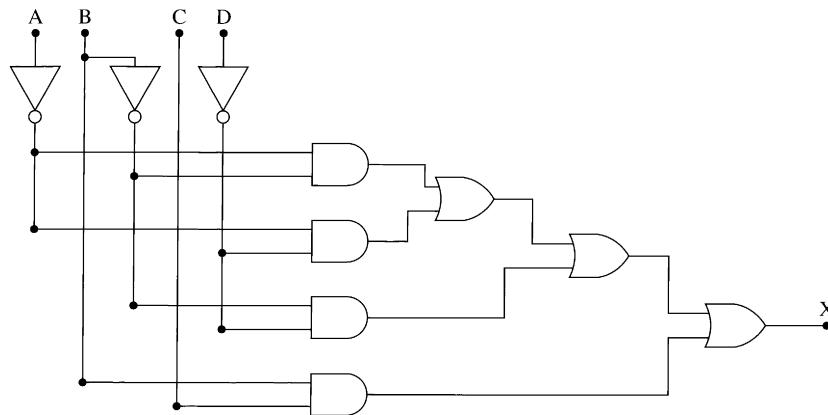

- E5-13.** (a) AND  
(b) OR

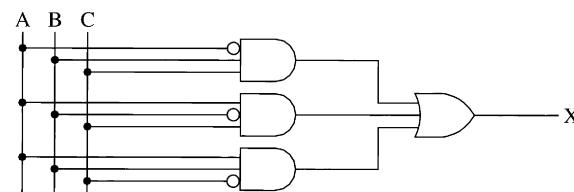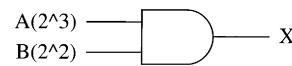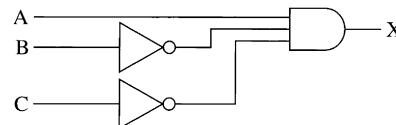**E5-14.****E5-15.****E5-16.**

- E5-17.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

- (a) U1b is bad (b) U1a is bad

- E5-18.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

- (a) U1a is bad (b) U1b is bad

- E5-19.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

- (a) U2b is bad (b) U3a is bad

- E5-20.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

- (a) U2b is bad (b) U1b is bad

- E5-21.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**


- (a) U1a is bad (b) U2a is bad

- E5-22.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

- (a) U3a is bad (b) U2a is bad

- E5-23.** Password for Options-Circuit Restrictions-Hide Component faults is: **wk5e**

- (a) 3  
(b) Gate 2  
(c)

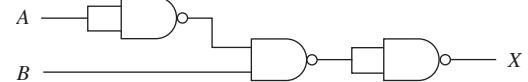


- E5-24.** Password for Options-Circuit Restrictions-Hide Component faults is: **wk5e**

- (a)  $X = (A'B)'$   
(b)  $X = A + B$   
(c) No  
(d) Yes, Gate 1

## Chapter 6

- 6-1.** (a) Exclusive-OR produces a HIGH output for one or the other input HIGH, but not both.  
(b) Exclusive-NOR produces a HIGH output for both inputs HIGH or both inputs LOW.

- 6-2.** (a) An OR outputs a HIGH for both inputs HIGH.  
(b) An AND outputs a LOW for both inputs LOW.


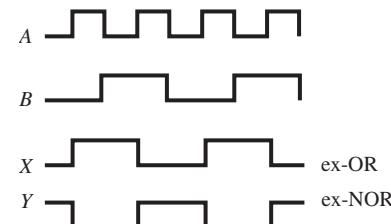
**6-3.**

$$W = \overline{AB} \cdot A + B = AB + \overline{A}\overline{B} \text{ (ex-NOR)}$$

$$X = AB + \overline{A} + \overline{B} = AB + \overline{A}\overline{B} \text{ (ex-NOR)}$$

$$Y = \overline{AB} \cdot \overline{\overline{AB}} = \overline{AB} + A\overline{B} \text{ (ex-OR)}$$

$$Z = \overline{\overline{AB} + A + B} = AB \text{ (neither)}$$

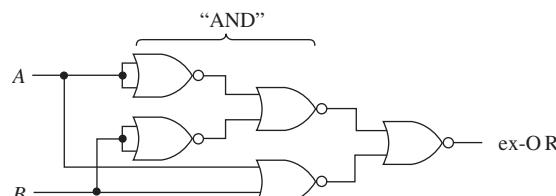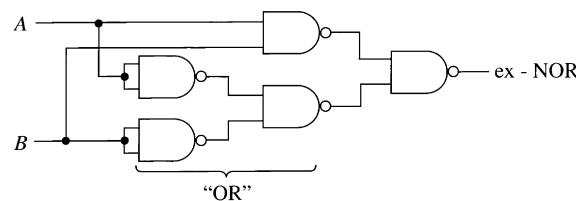**6-5.****6-6.**

$$6-7. X = \overline{(AB + \bar{A}\bar{B})} + \bar{A}\bar{B} = A\bar{B}$$

$$Y = \bar{A}\bar{B} + A\bar{B} \cdot AB = 1$$

$$6-8. X = \overline{ABC} + \overline{AB}\overline{BC}$$

$$X = \overline{ABC} + ABC$$

$$Y = \overline{AB} + C\overline{AB} + \overline{AB} + \overline{C}AB$$

$$Y = \overline{C} + AB$$

$$6-9. A7 = 1010\ 0111\ 0$$





$$4C = 0100\ 1100\ 0$$



$$79 = 0111\ 1001\ 0$$

$$F3 = 1111\ 0011\ 1$$

$$00 = 0000\ 0000\ 1$$

$$FF = 1111\ 1111\ 1$$

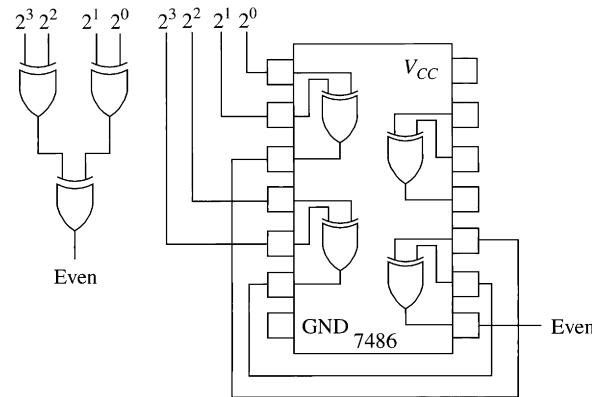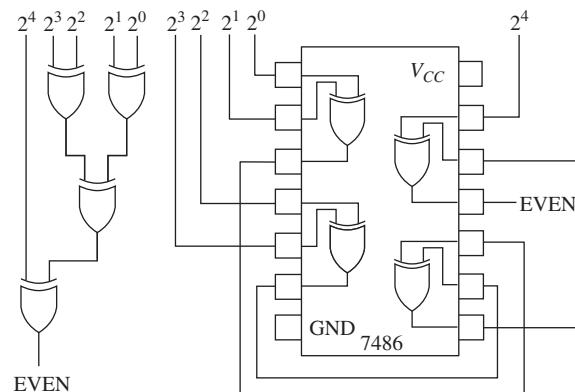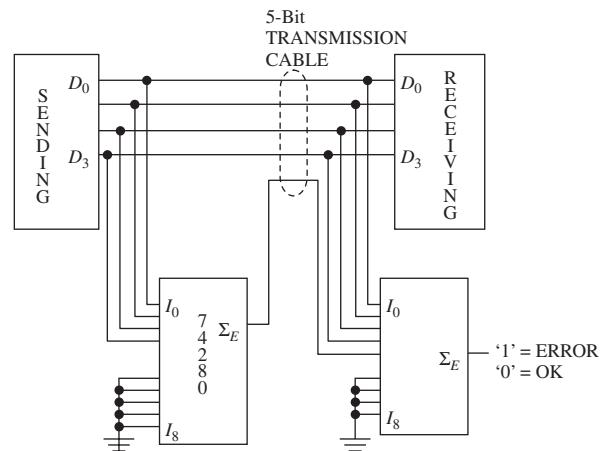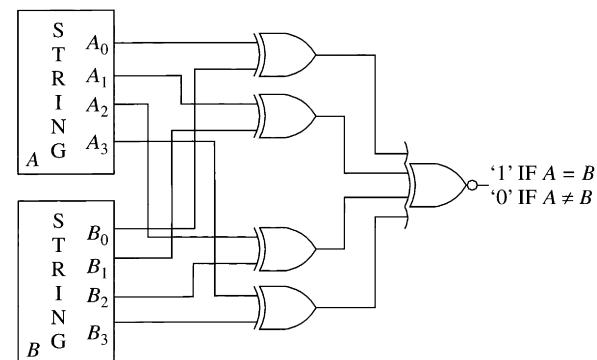**6-10.****6-11.****6-12. Odd****6-13.****6-14.****6-15. Yes; LOW**

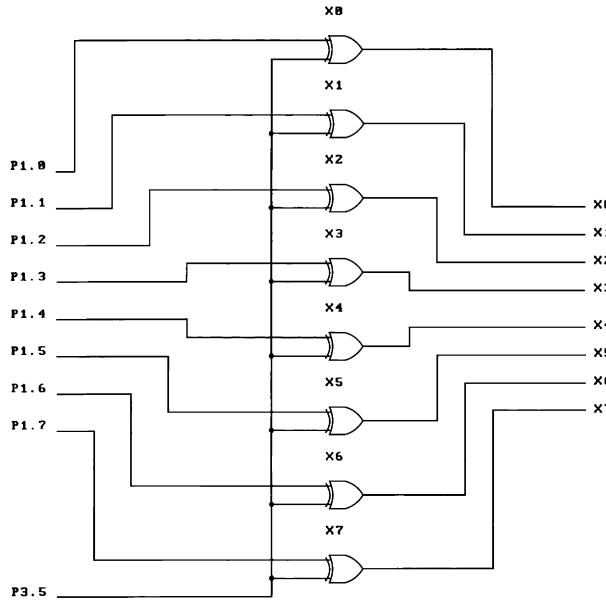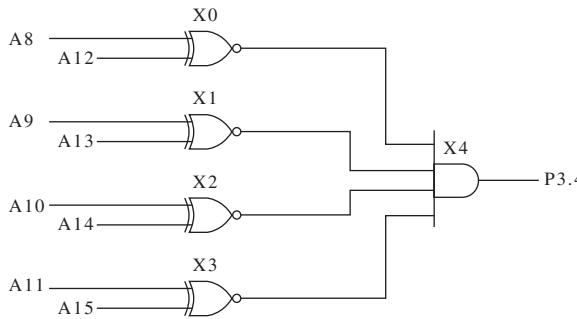**6-16.****6-17.****E6-1.** (a)  $X = 0, Y = 1$ (b)  $X = 0, Y = 1$ 

(c)

A	B	X	A	B	Y
0	0	0	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0
1	1	0	1	1	1

**E6-2.** (a) ex-OR (b) ex-NOR**E6-3.** Password for Options-Circuit Restrictions-Hide component faults is: **wk5e**

(a) Yes, because it is an Ex-OR.

(b) Gate 2

**E6-4.**  $X = (A'B + AB')C$ **E6-5.**  $X = (A'B + AB')BC = A'BC$ **E6-6.**  $X = A'B' + A'C' + ABC$ **E6-7.** Because they both have an odd number of ones**E6-8.** (a) Matching hex digits

(b) NOR

**Chapter 7**

- 7-1.** (a) 1001 (b) 1111 (c) 1 1100  
 (d) 100 0010 (e) 1100 1000  
 (f) 10010 0010 (g) 10100 1111  
 (h) 10110 0000

- 7-2.** (a) 0000 1011 (b) 0000 1011  
 (c) 0011 0000 (d) 0010 0011  
 (e) 0011 1110 (f) 0001 1001  
 (g) 00110001 (h) 0000 0111

- 7-3.** (a) 1 0101 (b) 10 1010 (c) 11 1100  
 (d) 1 0001 0001 (e) 1 1110 1100 0011  
 (f) 111 0111 0001 (g) 1 1001 0011  
 (h) 111 1110 1000 0001

- 7-4.** (a) 11 (b) 101 (c) 100 (d) 101  
 (e) 11001 (f) 10101 (g) 1101  
 (h) 10011

7-5.	+15	0000 1111	-1	1111 1111
	+14	0000 1110	-2	1111 1110
	+13	0000 1101	-3	1111 1101
	+12	0000 1100	-4	1111 1100
	+11	0000 1011	-5	1111 1011
	+10	0000 1010	-6	1111 1010
	+9	0000 1001	-7	1111 1001
	+8	0000 1000	-8	1111 1000
	+7	0000 0111	-9	1111 0111
	+6	0000 0110	-10	1111 0110
	+5	0000 0101	-11	1111 0101
	+4	0000 0100	-12	1111 0100
	+3	0000 0011	-13	1111 0011
	+2	0000 0010	-14	1111 0010
	+1	0000 0001	-15	1111 0001
	0	0000 0000		

- 7-6.**
- (a) 7 = 0000 0111

- (b) -7 = 1111 1001

- (c) 14 = 0000 1110

- (d) 36 = 0010 0100

- (e) -36 = 1101 1100

- (f) 66 = 0100 0010

- (g) -48 = 1101 0000

- (h) 112 = 0111 0000

- (i) -112 = 1001 0000

- (j) -125 = 1000 0011

- 7-7.**
- (a) 0001 0110 = +22

- (b) 0000 1111 = +15

- (c) 0101 1100 = +92

- (d) 1000 0110 = -122

- (e) 1110 1110 = -18

- (f) 1000 0001 = -127

- (g) 0111 1111 = +127

- (h) 1111 1111 = -1

- 7-8.**
- $2^{8-1} - 1 \text{ to } -2^{8-1} = 127 \text{ to } -128$

- $2^{16-1} - 1 \text{ to } -2^{16-1} = 32,767 \text{ to } -32,768$

- 7-9.** (a) 0000 1100 (b) 0000 0110  
 (c) 0011 0010 (d) 0000 1110  
 (e) 0000 1010 (f) 0011 1011  
 (g) 1111 0100 (h) 1010 1100

**7-10.**

Hex	Binary	Dec	Hex	Binary	Dec
0C	0000 1100	12	18	0001 1000	24
0D	0000 1101	13	19	0001 1001	25
0E	0000 1110	14	1A	0001 1010	26
0F	0000 1111	15	1B	0001 1011	27
10	0001 0000	16	1C	0001 1100	28
11	0001 0001	17	1D	0001 1101	29
12	0001 0010	18	1E	0001 1110	30
13	0001 0011	19	1F	0001 1111	31
14	0001 0100	20	20	0010 0000	32
15	0001 0101	21	21	0010 0001	33
16	0001 0110	22	22	0010 0010	34
17	0001 0111	23			

- 7-11.** (a) E (b) D (c) 21 (d) CA (e) 10C  
 (f) 162 (g) AB45 (h) A000

- 7-12.** (a) 6 (b) 6 (c) 15 (d) 8F (e) 23  
 (f) 8A (g) 2FFE (h) 40E8

**7-13.**  $100_{10} = 64H$


$2C8DH + 64H - 1 = 2CF0H$

**7-14.**  $0BD78H - 07A4BH + 1 = 0432EH$   
 $03000H - 02F80H + 1 = 00081H$   
 $0432EH + 00081H = 043AFH$

- 7-15.** b, c, e

- 7-16.** (a) 0001 0001 (b) 0010 1000  
 (c) 0001 0001 0101 (d) 1000 0101  
 (e) 0001 0000 0001 (f) 0101 1000  
 (g) 0001 0001 0000 (h) 0001 0000 0011

- 7-17.** For the LSB addition of two binary numbers.


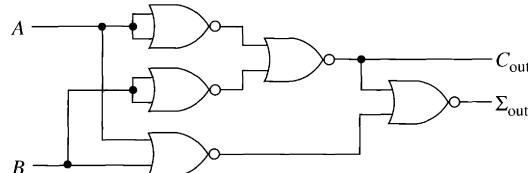
**7-18.**

**7-19.**  $\Sigma_0 = (A + B)\bar{AB} = A\bar{B} + \bar{A}B \dots \text{OK}$   
 $C_0 = (A + B)(\bar{A}\bar{B})(A + B) =$   
 $A\bar{B} + \bar{A}B \dots \text{NO}$


**7-20.** From Figure 7-5(c),

$$C_{\text{out}} = \bar{A}BC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC.$$

$C_{\text{out}} = AB + AC + BC$ , which matches Figure 7-9.

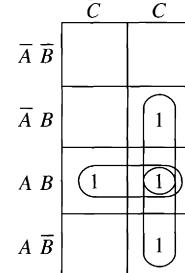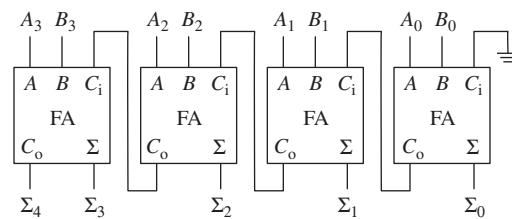
**7-21.**

- 7-22.** There is no carry-in to the LSB of the low-order adder, so  $C_{\text{in}}$  must be grounded to ensure it is zero. The carry-out of the low-order adder must be connected to the carry-in of the high-order adder to pass any carry from the  $2^3$  addition over to the  $2^4$  addition.

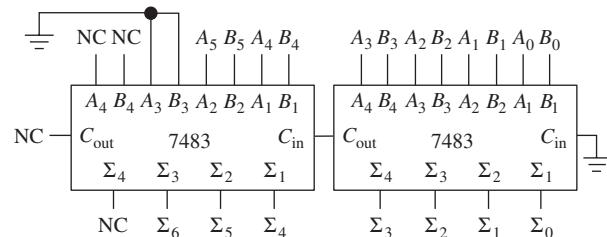**7-23.**

- 7-24.** When using more than one adder, IC to add long binary strings, the fast-lookahead-carry speeds up the addition by providing the carry-in to the higher-order ICs almost simultaneously with the binary inputs to be added.

7-25.

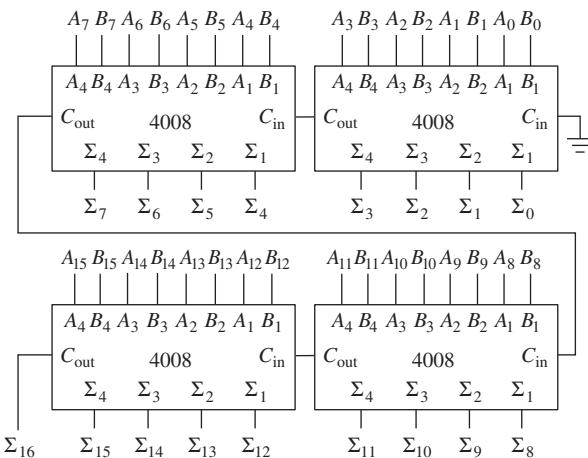


7-26. Reverse the switch (up to add, down to subtract). Also, put an inverter on input line to  $C_{in}$  of the LSB.

- 7-27. The Ex-OR gate third from right is bad.  
Also, the full-adder fourth from right is bad.
- 7-28. The B inputs should be  $B_3 = 0, B_2 = 0, B_1 = 1, B_0 = 0$ . Also, the function-select inputs should be  $S_3 = 1, S_2 = 0, S_1 = 0, S_0 = 1$ .


7-29.  $S_3 - S_0 = 0100$ .

- (a) 1110 (b) 0001


7-30.

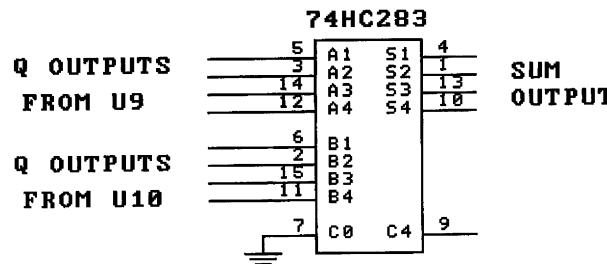

7-31.

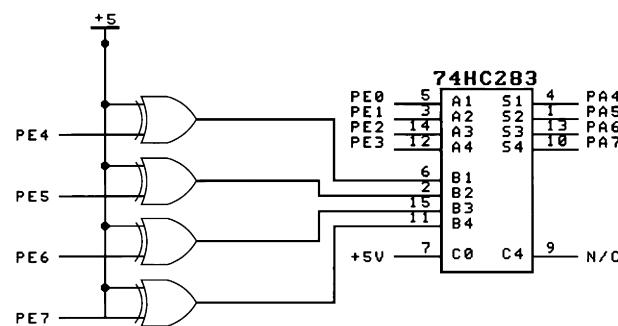

7-32.

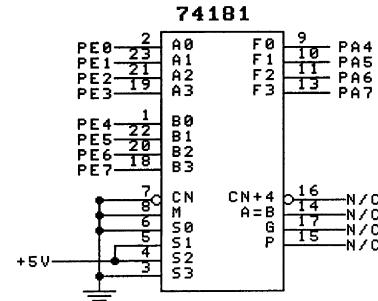

- E7-1. (a) 3 inputs, 2 outputs  
(b) Full adder truth table  
(c) The number of HIGH inputs is odd. The number of HIGH inputs is 2 or more.

- E7-2. (a) Ground it  
(b)  $0111 + 0110 = 1101$


- E7-3. (a) 0011 1011  
(b) 0111 0000

- E7-4. (a) 0 0111 1101 (1 = ON)  
(b) 1 0001 1001 (1 = ON)




- E7-5. (a) 1 0011 (1 = ON)  
(b) 1 0111 (1 = ON)

## Chapter 8

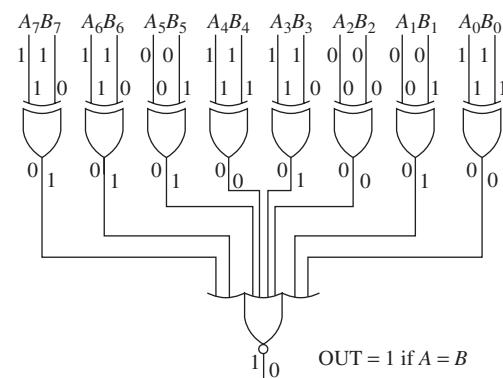- 8-1. (a) See top numbers.  
(b) See lower numbers.



- 8-2.** (a) See top numbers.  
 (b) See lower numbers.

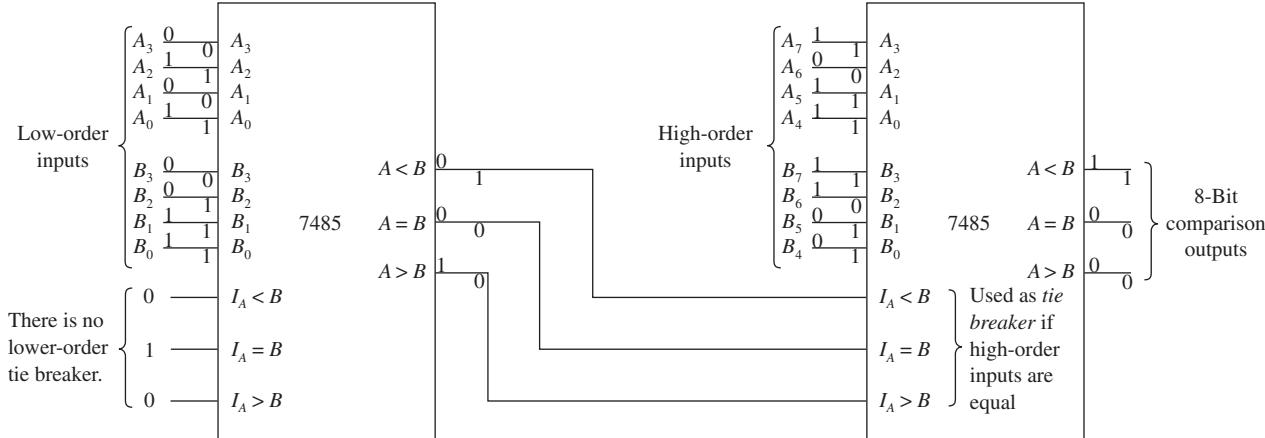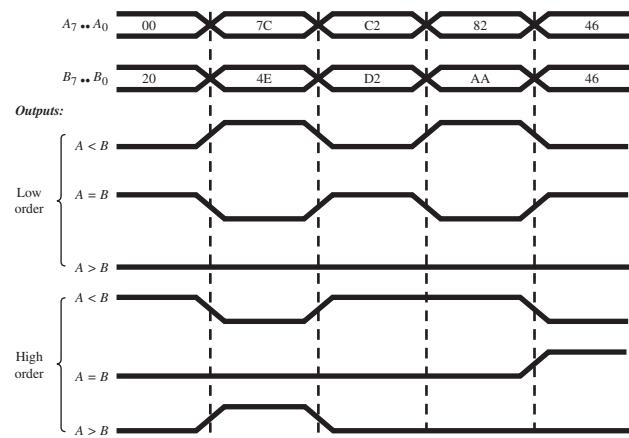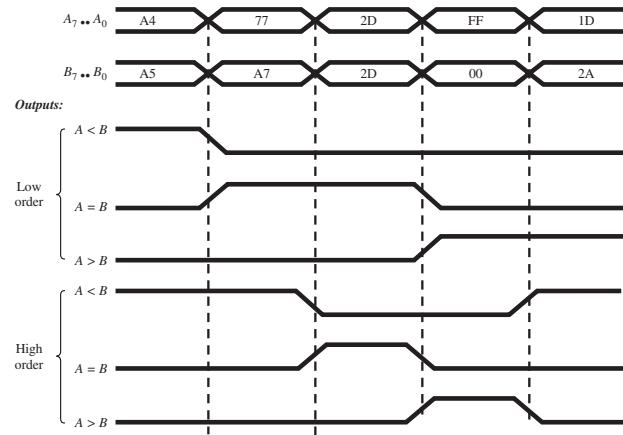**8-3. (a)****8-3. (b)**

- 8-4.** A decoder has a coded multibit number such as octal or hex at its input. It has several outputs, only one of which is active, corresponding to the translation of the code at its input.

**8-5.**

$2^3$	$2^2$	$2^1$	$2^0$	$\bar{0}$	$\bar{1}$	$\bar{2}$	$\bar{3}$	$\bar{4}$	$\bar{5}$	$\bar{6}$	$\bar{7}$	$\bar{8}$	$\bar{9}$
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	1	1	0	1	1	1	1
0	1	1	1	1	1	1	1	1	1	0	1	1	1
1	0	0	0	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	1

$$\bar{8}-6. \quad \bar{E}_1 = 0, \bar{E}_2 = 0, E_3 = 1$$

That input is a “don’t care” and will have no effect on the output for that particular table entry.

- 8-7.** Active LOW outputs are 0 when selected. Active-HIGH outputs are 1 when selected.

- 8-8.** (a)  $\bar{0} \bar{1} \bar{2} \bar{3} \bar{4} \bar{5} \bar{6} \bar{7} = 10111111$   
 (b)  $\bar{0} \bar{1} \bar{2} \bar{3} \bar{4} \bar{5} \bar{6} \bar{7} = 11111111$

- 8-9.** Time interval      Low output pulse at:

$t_0 - t_1$	None ( $E_3$ disabled)
$t_1 - t_2$	None ( $E_3$ disabled)
$t_2 - t_3$	5
$t_3 - t_4$	4
$t_4 - t_5$	3
$t_5 - t_6$	2
$t_6 - t_7$	1
$t_7 - t_8$	0
$t_8 - t_9$	7
$t_9 - t_{10}$	6
$t_{10} - t_{11}$	5
$t_{11} - t_{12}$	None ( $E_3$ disabled)
$t_{12} - t_{13}$	None ( $E_3$ disabled)