

CHAPTER 2

2-1. (a) Applying the voltage divider equation (2-10)

$$\frac{1.0}{10} = \frac{R_1}{R_1 + R_2 + R_3}$$

$$\frac{4.0}{10} = \frac{R_2}{R_1 + R_2 + R_3}$$

$$V_3 = 10.0\text{V} - 1.0\text{V} - 4.0\text{V} = 5.0\text{V}$$

$$\frac{5.0}{10} = \frac{R_3}{R_1 + R_2 + R_3}$$

Dividing the first equation by the second, gives

$$R_1/R_2 = 1.0/4.0$$

Similarly,

$$R_2/R_3 = 4.0/5.0$$

Letting $R_1 = 250\ \Omega$, $R_2 = 250 \times 4.0 = 1.0\ \text{k}\Omega$,

and $R_3 = 1.0\ \text{k}\Omega \times 5.0/4.0 = 1.25\ \text{k}\Omega$. Use a $1.0\ \text{k}\Omega$ resistor and a $250\ \text{k}\Omega$ resistor in series. The $500\ \text{k}\Omega$ resistor is not used.

(b) $V_3 = IR_3 = 10.0\text{V} - 1.0\text{V} - 4.0\text{V} = 5.0\text{V}$

(c) $I = V/(R_1 + R_2 + R_3) = 10.0\text{V}/(250\ \Omega + 1000\ \Omega + 1250\ \Omega) = 0.004\text{A}$ (4.0 mA)

(d) $P = IV = 0.004\text{A} \times 10.0\text{V} = 0.04\text{W}$ (Equation 2-2)

2-2. (a) From Equation 2-10, $V_2 = 15 \times 400/(200 + 400 + 2000) = 2.31\text{V}$

(b) $P = V_2^2/R_2 = (2.31)^2/400 = 0.013\text{W}$

(c) Total $P = V^2/R_s = (15)^2/2600 = 0.087\text{W}$

$$\text{Percentage loss in } R_2 = (0.013/0.087) \times 100 = 15\%$$

$$2-3. \quad V_{2,4} = 24.0 \times [(2.0 + 4.0) \times 10^3] / [(1.0 + 2.0 + 4.0) \times 10^3] = 20.6 \text{ V}$$

With the meter in parallel across contacts 2 and 4,

$$\frac{1}{R_{2,4}} = \frac{1}{(2.0 + 4.0) \text{ k}\Omega} + \frac{1}{R_M} = \frac{R_M + 6.0 \text{ k}\Omega}{R_M \times 6.0 \text{ k}\Omega}$$

$$R_{2,4} = (R_M \times 6.0 \text{ k}\Omega) / (R_M + 6.0 \text{ k}\Omega)$$

$$(a) \quad R_{2,4} = (4.0 \text{ k}\Omega \times 6.0 \text{ k}\Omega) / (4.0 \text{ k}\Omega + 6.0 \text{ k}\Omega) = 2.40 \text{ k}\Omega$$

$$V_M = (24.0 \text{ V} \times 2.40 \text{ k}\Omega) / (1.00 \text{ k}\Omega + 2.40 \text{ k}\Omega) = 16.9 \text{ V}$$

$$\text{rel error} = \frac{16.9 \text{ V} - 20.6 \text{ V}}{20.6 \text{ V}} \times 100\% = -18\%$$

Proceeding in the same way, we obtain (b) -1.2% and (c) -0.2%

2-4. Applying Equation 2-19, we can write

$$(a) \quad -1.0\% = -\frac{1000 \Omega}{(R_M - 1000 \Omega)} \times 100\%$$

$$R_M = (1000 \times 100 - 1000) \Omega = 99000 \Omega \text{ or } 99 \text{ k}\Omega$$

$$(b) \quad -0.1\% = -\frac{1000 \Omega}{(R_M - 1000 \Omega)} \times 100\%$$

$$R_M = 999 \text{ k}\Omega$$

2-5. Resistors R_2 and R_3 are in parallel, the parallel combination R_p is given by Equation 2-17

$$R_p = (500 \times 250) / (500 + 250) = 166.67 \Omega$$

(a) This 166.67Ω R_p is in series with R_1 and R_4 . Thus, the voltage across R_1 is

$$V_1 = (15.0 \times 250) / (250 + 166.67 + 1000) = 2.65 \text{ V}$$

$$V_2 = V_3 = 15.0 \text{ V} \times 166.67/1416.67 = 1.76 \text{ V}$$

$$V_4 = 15.0 \text{ V} \times 1000/1416.67 = 10.59 \text{ V}$$

$$(b) \quad I_1 R_1 = V_1 = 2.647 \text{ V} \quad I_1 = 2.647/250 = 0.01059 \text{ A} \quad (1.06 \times 10^{-2} \text{ A})$$

$$I_2 = 1.76 \text{ V}/500 \text{ } \Omega = 3.5 \times 10^{-3} \text{ A}$$

$$I_3 = 1.76 \text{ V}/250 \text{ } \Omega = 7.0 \times 10^{-3} \text{ A}$$

$$I_4 = 10.59 \text{ V}/1000 \text{ } \Omega = 0.01059 \text{ A} \quad (1.06 \times 10^{-2} \text{ A})$$

$$(c) \quad P = IV = 1.76 \text{ V} \times 7.0 \times 10^{-3} \text{ A} = 1.2 \times 10^{-2} \text{ W}$$

(d) Since point 3 is at the same potential as point 2, the voltage between points 3 and 4 (V') is the sum of the drops across the 166.67 Ω and the 1000 Ω resistors. Or,

$$V' = 1.76 \text{ V} + 10.59 \text{ V} = 12.35 \text{ V. It is also the source voltage minus the } V_1$$

$$V' = 15.0 - 2.65 = 12.35 \text{ V}$$

2-6. The resistance between points 1 and 2 is the parallel combination of R_B and R_C

$$R_{1,2} = 3.0 \text{ k}\Omega \times 4.0 \text{ k}\Omega / (3.0 \text{ k}\Omega + 4.0 \text{ k}\Omega) = 1.71 \text{ k}\Omega$$

Similarly the resistance between points 2 and 3 is

$$R_{2,3} = 2.0 \text{ k}\Omega \times 1.0 \text{ k}\Omega / (2.0 \text{ k}\Omega + 1.0 \text{ k}\Omega) = 0.667 \text{ k}\Omega$$

These two resistors are in series with R_A for a total series resistance R_T of

$$R_T = 1.71 \text{ k}\Omega + 0.667 \text{ k}\Omega + 2.0 \text{ k}\Omega = 4.38 \text{ k}\Omega$$

$$I = 24 / (4380 \text{ } \Omega) = 5.5 \times 10^{-3} \text{ A}$$

$$(a) \quad P_{1,2} = I^2 R_{1,2} = (5.5 \times 10^{-3})^2 \times 1.71 \times 10^3 = 0.052 \text{ W}$$

$$(b) \quad \text{As above } I = 5.5 \times 10^{-3} \text{ A} \quad (5.5 \text{ mA})$$

$$(c) \quad V_A = IR_A = 5.5 \times 10^{-3} \text{ A} \times 2.0 \times 10^3 \text{ } \Omega = 11.0 \text{ V}$$

$$(d) V_D = 24 \times R_{2,3}/R_T = 24 \times 0.667/4.38 = 3.65 \text{ V}$$

$$(e) V_{5,4} = 24 - V_A = 24 - 11.0 = 13 \text{ V}$$

2-7. With the standard cell in the circuit,

$$V_{\text{std}} = V_b \times AC/AB \quad \text{where } V_b \text{ is the battery voltage}$$

$$1.018 = V_b \times 84.3/AB$$

With the unknown voltage V_x in the circuit,

$$V_x = V_b \times 44.2/AB$$

Dividing the third equation by the second gives,

$$\frac{1.018 \text{ V}}{V_x} = \frac{84.3 \text{ cm}}{44.3 \text{ cm}}$$

$$V_x = 1.018 \times 44.3 \text{ cm}/84.3 \text{ cm} = 0.535 \text{ V}$$

$$2-8. \quad E_r = -\frac{R_S}{R_M + R_S} \times 100\%$$

$$\text{For } R_S = 20 \text{ } \Omega \text{ and } R_M = 10 \text{ } \Omega, \quad E_r = -\frac{20}{10 + 20} \times 100\% = -67\%$$

$$\text{Similarly, for } R_M = 50 \text{ } \Omega, \quad E_r = -\frac{20}{50 + 20} \times 100\% = -29\%$$

The other values are shown in a similar manner.

$$2-9. \quad \text{Equation 2-20 is } E_r = -\frac{R_{\text{std}}}{R_L + R_{\text{std}}} \times 100\%$$

$$\text{For } R_{\text{std}} = 1 \text{ } \Omega \text{ and } R_L = 1 \text{ } \Omega, \quad E_r = -\frac{1 \text{ } \Omega}{1 \text{ } \Omega + 1 \text{ } \Omega} \times 100\% = -50\%$$

$$\text{Similarly for } R_L = 10 \Omega, E_r = -\frac{1 \Omega}{10 \Omega + 1 \Omega} \times 100\% = -9.1\%$$

The other values are shown in a similar manner.

2-10. (a) $R_s = V/I = 1.00 \text{ V}/20 \times 10^{-6} \text{ A} = 50000 \Omega$ or 50 k Ω

(b) Using Equation 2-19

$$-1\% = -\frac{50 \text{ k}\Omega}{R_M + 50 \text{ k}\Omega} \times 100\%$$

$$R_M = 50 \text{ k}\Omega \times 100 - 50 \text{ k}\Omega = 4950 \text{ k}\Omega \text{ or } \approx 5 \text{ M}\Omega$$

2-11. $I_1 = 90/(25 + 5000) = 1.791 \times 10^{-2} \text{ A}$

$$I_2 = 90/(45 + 5000) = 1.784 \times 10^{-2} \text{ A}$$

$$\% \text{ change} = [(1.784 \times 10^{-2} \text{ A} - 1.791 \times 10^{-2} \text{ A}) / 1.791 \times 10^{-2} \text{ A}] \times 100\% = -0.4\%$$

2-12. $I_1 = 12.5/420 = 2.976 \times 10^{-2} \text{ A}$

$$I_2 = 12.5/440 = 2.841 \times 10^{-2} \text{ A}$$

$$\% \text{ change} = [(2.841 \times 10^{-2} - 2.976 \times 10^{-2}) / 2.976 \times 10^{-2}] \times 100\% = -4.5\%$$

2-13. $i = I_{\text{init}} e^{-t/RC}$ (Equation 2-35)

$$RC = 25 \times 10^6 \Omega \times 0.2 \times 10^{-6} \text{ F} = 5.00 \text{ s} \quad I_{\text{init}} = 24\text{V}/(25 \times 10^6 \Omega) = 9.6 \times 10^{-7} \text{ A}$$

$$i = 9.6 \times 10^{-7} e^{-t/5.00} \text{ A} \text{ or } 0.96 \times e^{-t/5.0} \mu\text{A}$$

t, s	$i, \mu\text{A}$	t, s	$i, \mu\text{A}$
0.00	0.96	1.0	0.786
0.010	0.958	10	0.130
0.10	0.941		

2-14. $v_C = V_C e^{-t/RC}$ (Equation 2-40)

$$v_C/V_C = 1.00/100 \text{ for discharge to 1\%}$$

$$0.0100 = e^{-t/RC} = e^{-t/(R \times 0.025 \times 10^{-6})}$$

$$\ln 0.0100 = -4.61 = -t/(2.5 \times 10^{-8} R)$$

$$t = 4.61 \times 2.5 \times 10^{-8} R = 1.15 \times 10^{-7} R$$

(a) When $R = 10 \text{ M}\Omega$ or $10 \times 10^6 \Omega$, $t = 1.15 \text{ s}$

(b) Similarly, when $R = 1 \text{ M}\Omega$, $t = 0.115 \text{ s}$

(c) When $R = 1 \text{ k}\Omega$, $t = 1.15 \times 10^{-4} \text{ s}$

2-15. (a) When $R = 10 \text{ M}\Omega$, $RC = 10 \times 10^6 \Omega \times 0.025 \times 10^{-6} \text{ F} = 0.25 \text{ s}$

(b) $RC = 1 \times 10^6 \times 0.025 \times 10^{-6} = 0.025 \text{ s}$

(c) $RC = 1 \times 10^3 \times 0.025 \times 10^{-6} = 2.5 \times 10^{-5} \text{ s}$

2-16. Parts (a) and (b) are given in the spreadsheet below. For part (c), we calculate the quantities from

$$i = I_{\text{init}} e^{-t/RC}, v_R = iR, \text{ and } v_C = 25 - v_R$$

For part (d) we calculate the quantities from

$$i = \frac{-v_C}{R} e^{-t/RC}, v_R = iR, \text{ and } v_C = -v_R$$

The results are given in the spreadsheet.

	A	B	C	D	E	F	G	H	I
1	Problem 2-16								
2	R	5.00E+04	ohms						
3	C	3.50E-08	farads						
4	V	25	Volts						
6	(a)								
7	RC	1.75E-03	s						
8	(b)								
9	i_{init}	5.00E-04	A						
10			t, s	$i, \mu A$	v_R, V	v_C, V			
11			0	500	25	0.0			
12			1	282	14	11			
13			2	159	8.0	17			
14			3	90	4.5	20			
15			4	51	2.5	22			
16			5	29	1.4	24			
17			10	2	0.08	24.9			
18									
19	(c)								
20			t, s	$i, \mu A$	v_R, V	v_C, V			
21			0	-498	-24.9	24.9			
22			1	-281	-14.1	14.1			
23			2	-159	-7.9	7.9			
24			3	-90	-4.5	4.5			
25			4	-51	-2.5	2.5			
26			5	-29	-1.4	1.4			
27			10	-1.6	-0.08	0.08			
28	Spreadsheet Documentation								
29	Cell B7=B2*B3				Cell D20=-(\$F\$17/\$B\$2)*1000000*EXP(-C20/\$B\$7*0.001)				
30	Cell B9=B4/B2				Cell E20=D20*0.000001*\$B\$2				
31	Cell D11=\$B\$9*1000000*EXP(-C11/\$B\$7*0.001)				Cell F20=-E20				
32	Cell E11=\$B\$2*0.000001*D11								
33	Cell F11=\$B\$4-E11								

2-17. Proceeding as in Problem 2-16, the results are in the spreadsheet

	A	B	C	D	E	F	G	H	I
1	Problem 2-17								
2	<i>R</i>	2.00E+07	Ω						
3	<i>C</i>	5.00E-08	F						
4	<i>V</i>	15	V						
6	(a)								
7	<i>RC</i>	1.00	s						
8	(b)								
9	<i>I</i> _{init}	7.50E-07							
10			<i>t</i> , s	<i>i</i> , μA	<i>v</i> _R , V	<i>v</i> _C , V			
11			0	0.75	15.0	0.0			
12			1	0.28	5.5	9.5			
13			2	0.10	2.0	13.0			
14			3	3.7E-02	0.75	14.3			
15			4	1.4E-02	0.27	14.7			
16			5	5.1E-03	0.10	14.9			
17			10	3.4E-05	0.00	15.0			
18									
19	(c)		<i>t</i> , s	<i>i</i> , μA	<i>v</i> _R , V	<i>v</i> _C , V			
20			0	-0.75	-15.0	15.0			
21			1	-0.28	-5.5	5.5			
22			2	-0.10	-2.0	2.0			
23			3	-3.7E-02	-0.75	0.75			
24			4	-1.4E-02	-0.27	0.27			
25			5	-5.1E-03	-0.10	0.10			
26			10	-3.4E-05	0.00	0.00			
27									
28	Spreadsheet Documentation								
29	Cell B7=B2*B3				Cell D20=-(F\$17/\$B\$2)*1000000*EXP(-C20/\$B\$7)				
30	Cell B9=B4/B2				Cell E20=D20*0.000001*\$B\$2				
31	Cell D11=\$B\$9*1000000*EXP(-C11/\$B\$7)				Cell F20=-E20				
32	Cell E11=\$B\$2*0.000001*D11								
33	Cell F11=\$B\$4-E11								

2-18. In the spreadsheet we calculate X_C , Z , and ϕ from

$$X_C = 2/2\pi fC, Z = \sqrt{R^2 + X_C^2}, \text{ and } \phi = \text{arc tan}(X_C/R)$$

	A	B	C	D	E	F	G
1	Problem 2-18						
2		f , Hz	R , Ω	C , F	X_C , Ω	Z , Ω	ϕ , degrees
3	(a)	1	30000	3.30E-08	4.82E+06	4.8E+06	-90
4	(b)	1.00E+03	30000	3.30E-08	4.82E+03	3.0E+04	-9.1
5	(c)	1.00E+06	30000	3.30E-09	48.2	3.0E+04	-0.1
6	(d)	1	300	3.30E-09	4.82E+07	4.8E+07	-90.0
7	(e)	1.00E+03	300	3.30E-09	4.82E+04	4.8E+04	-89.6
8	(f)	1.00E+06	300	3.30E-09	48.2	3.0E+02	-9.1
9	(g)	1	3000	3.30E-07	4.82E+05	4.8E+05	-89.6
10	(h)	1.00E+03	3000	3.30E-07	4.82E+02	3.0E+03	-9.1
11	(i)	1.00E+06	3000	3.30E-07	0.48	3.0E+03	0.0
12							
13	Spreadsheet Documentation						
14	Cell E3=1/(2*PI()*B3*D3)						
15	Cell F3=SQRT(C3^2+E3^2)						
16	Cell G3=DEGREES(-ATAN(E3/C3))						


2-19. Let us rewrite Equation 2-54 in the form

$$y = \frac{(V_p)_o}{(V_p)_i} = \frac{1}{\sqrt{(2\pi fRC)^2 + 1}}$$

$$y^2(2\pi fRC)^2 + y^2 = 1$$

$$f = \frac{1}{2\pi RC} \sqrt{\frac{1}{y^2} - 1} = \frac{1}{2\pi RC} \sqrt{\frac{1-y^2}{y^2}}$$

The spreadsheet follows

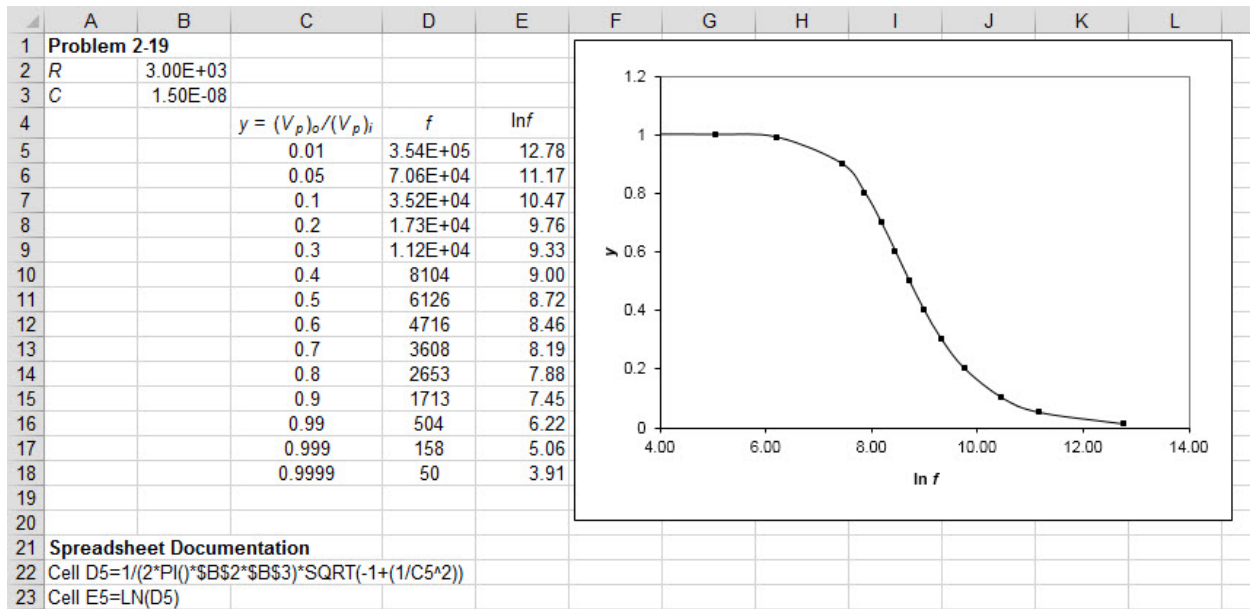

2-20. By dividing the numerator and denominator of the right side of Equation 2-53 by R , we obtain

$$y = \frac{(V_p)_o}{(V_p)_i} = \frac{1}{\sqrt{1 + (1/2\pi fRC)^2}}$$

Squaring this equation yields

$$y^2 + y^2/(2\pi fRC)^2 = 1$$

$$2\pi fRC = \sqrt{\frac{y^2}{1-y^2}}$$

$$f = \frac{1}{2\pi RC} \sqrt{\frac{y^2}{1-y^2}}$$

The results are shown in the spreadsheet that follows.

